

ECE102 (Winter 2011), Solution of the Final

Problem 1. Find the mid-frequency gain of the circuit below with identical transistors with $V_{OV} = 0.5$ V, $I_D = 50$ μ A, and $V_A = 10$ V.

This is a PMOS Cascode amplifier (Q1 and Q2) with an active load (Q3).

$$g_{m1} = g_{m2} = g_{m3} = g_m = \frac{2I_D}{V_{OV}} = \frac{2 \times 50 \times 10^{-6}}{0.5} = 2 \times 10^{-4} \text{ A/V}$$

$$r_{o1} = r_{o2} = r_{o3} = r_o = \frac{V_A}{I_D} = \frac{10}{50 \times 10^{-6}} = 200 \text{ k}$$

Replacing Q3 (active load) with its value: $r_{o3} = 20$ k, we get the circuit to the right above. For a Cascode amplifier:

$$A_{vo} \approx -g_{m1}g_{m2}r_{o1}r_{o2} = -1,600$$

$$R_o = r_{o1} + r_{o2} + g_{m2}r_{o1}r_{o2} = 8,400 \text{ k}$$

$$A_v = A_{vo} \frac{R_L}{R_o + R_L} = -1,600 \times \frac{200}{200 + 8,400} = -37.2$$


Alternatively, Q2 is a CG amplifier and CS is a CS amplifier:

$$\frac{v_o}{v_x} = A_{vo} = g_{m2}(r_{o2} \parallel R_D) = 2 \times 10^{-4}(200 \text{ k} \parallel 200 \text{ k}) = -20$$


$$R_{L1} = R_{i2} = \frac{r_{o2} + r_{o3}}{1 + g_{m2}r_{o2}} = 9.76 \text{ k}$$

$$\frac{v_x}{v_i} = A_{v1} = -g_{m1}(r_{o1} \parallel R_{L1}) = -18.6$$

$$\frac{v_o}{v_i} = \frac{v_o}{v_x} \times \frac{v_x}{v_i} = -37.2$$

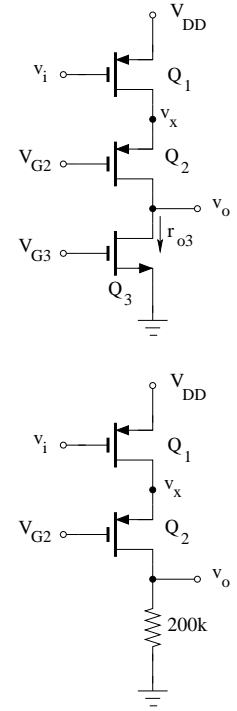

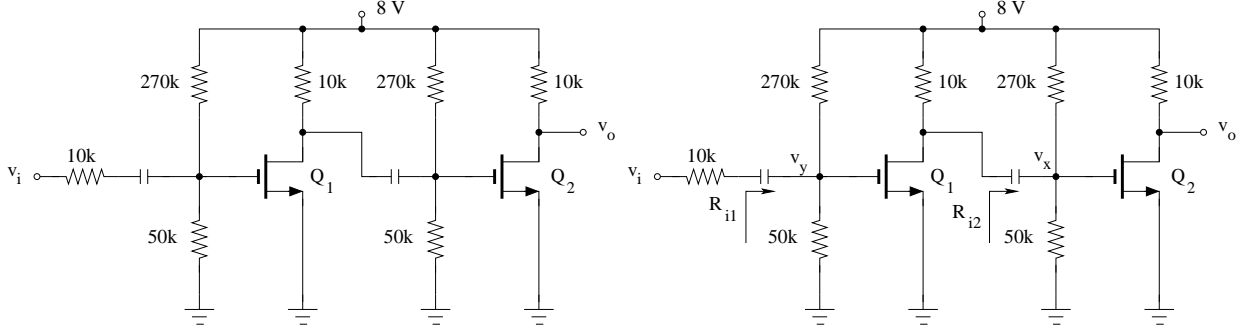Problem 2. Find v_o/v_i in the circuit below with large capacitors and identical transistors with $\mu_n C_{ox}(W/L) = 2.4 \text{ mA/V}^2$, $V_t = 0.75 \text{ V}$ and $\lambda = 0$.



Bias: We need to calculate I_D and V_{OV} first from bias values. Note that the bias circuits for both transistors are the same:

$$V_{G1} = V_{G2} = \frac{50 \text{ k}}{270 \text{ k} + 50 \text{ k}} \times 8 = 1.25 \text{ V}$$

$$V_{GS1} = V_{GS2} = V_G - 0 = 1.25 \text{ V}$$

$$V_{OV1} = V_{OV2} = V_{GS1} - V_t = 0.5 \text{ V}$$

$$I_{D1} = I_{D2} = 0.5 \mu_n C_{ox} (W/L) V_{ov}^2 = 0.5 \times 2.4 \times 10^{-3} \times (0.5)^2 = 0.3 \text{ mA}$$

$$g_{m1} = g_{m2} = \frac{2I_{D1}}{V_{OV1}} = 1.2 \text{ mA/V} \quad \text{and} \quad r_o \rightarrow \infty$$

Since $V_{OV} > 0$ and $V_{DS} = 8 - I_D R_D = 5 > V_{OV}$, both transistors are in saturation.

To find the gain, we start with Q2 (load side). Q2 is a CS amplifier with:

$$\frac{v_o}{v_x} = A_{v2} = -g_m (r_o \parallel R_D \parallel R_L) = -g_m R_D = -1.2 \times 10^{-3} \times 10 \times 10^3 = -12$$

$$R_{i2} = 50 \text{ k} \parallel 270 \text{ k} = 42.2 \text{ k}$$

R_{i2} is the load for Q1. Q1 is also a CS amplifier:

$$\frac{v_x}{v_y} = A_{v1} = -g_m (r_o \parallel R_D \parallel R_L) = -g_m (R_D \parallel R_{i2})$$

$$\frac{v_x}{v_y} = -1.2 \times 10^{-3} \times (10 \times 10^3 \parallel 42.2 \times 10^3) = -9.7$$

$$R_{i1} = 50 \text{ k} \parallel 270 \text{ k} = 42.2 \text{ k}$$


Finally, v_y/v_i can be found from the voltage divider formula:

$$\frac{v_y}{v_i} = \frac{R_{i1}}{R_{i1} + 10 \text{ k}} = 0.81$$

$$\frac{v_o}{v_i} = \frac{v_o}{v_x} \times \frac{v_x}{v_y} \times \frac{v_y}{v_i} = (-12)(-9.7)(0.81) = 94.3$$

Problem 3. Find v_o/v_i in the circuit below with $\mu_n C_{ox}(W/L) = \mu_p C_{ox}(W/L) = 8 \text{ mA/V}^2$ and $|V_t| = 1 \text{ V}$, and $\lambda = 0.1 \text{ 1/V}$. Ignore channel-width modulation in biasing calculations.

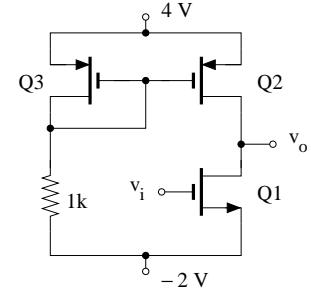Q1 is a CS amplifier biased by a current mirror (Q2 and Q3). Q2 is also the active load for Q1. Bias values are needed to compute g_m and r_o of the transistors.



$$I_{D3} = 0.5\mu_p C_{ox}(W/L)V_{OV3}^2 = 4 \times 10^{-3}V_{OV3}^2$$

$$\text{GS3-KVL} \quad 4 = V_{SG3} + 10^3 I_{D3} - 2 = V_{OV3} + |V_t| + 10^3 I_{D3} - 2$$

$$5 = V_{OV3} + 10^3 I_{D3}$$

$$5 = V_{OV3} + 10^3 \times 4 \times 10^{-3} V_{OV3}^2$$

$$4V_{OV3}^2 + V_{OV3} - 5 = 0 \quad \rightarrow \quad V_{OV3} = 1 \text{ V}$$

$$I_{D3} = 4 \times 10^{-3} V_{OV3}^2 = 4 \text{ mA}$$

Since Q2 and Q3 form a current mirror and $(W/L)_2 = (W/L)_3$, $I_{D2} = I_{D3} = 4 \text{ mA}$ and $V_{OV3} = V_{OV2} = 1 \text{ V}$.

Furthermore, $I_{D1} = I_{D2} = 4 \text{ mA}$ and since $\mu_n C_{ox}(W/L) = \mu_p C_{ox}(W/L)$, $V_{OV1} = V_{OV2} = 1 \text{ V}$. Therefore,

$$g_{m1} = g_{m2} = \frac{2I_{D1}}{V_{OV}} = \frac{2 \times 4 \times 10^{-3}}{1} = 8 \times 10^{-3} \text{ A/V}$$

$$r_{o1} = r_{o2} = \frac{V_A}{I_{D1}} = \frac{1}{\lambda I_D} = \frac{1}{0.1 \times 4 \times 10^{-3}} = 2.5 \text{ k}$$

Q1 is a CS amplifier with Q2 as its active load ($R_D = r_{o2} = 2.5 \text{ k}$). Thus,

$$\frac{v_o}{v_i} = A_v = -g_m(r_{o1} \parallel R_D) = 8 \times 10^{-3} \times (2.5 \text{ k} \parallel 2.5 \text{ k}) = -10$$

Problem 4. Consider the circuit below $\mu_p C_{ox}(W/L) = 3.2 \text{ mA/V}^2$, $V_t = -1 \text{ V}$ and $\lambda = 0$. A) Find R such that $I_D = 200 \text{ } \mu\text{A}$. B) Find the mid-frequency gain. C) Find f_L .

Starting with the Ohm's Law across the 20k resistor:

$$10 - V_S = 20 \times 10^3 I_D$$


$$V_S = 10 - 20 \times 10^3 \times 200 \times 10^{-6} = 10 - 4 = 6 \text{ V}$$

$$200 \times 10^{-6} = I_D = 0.5 \mu_p C_{ox}(W/L) V_{OV}^2 = 1.6 \times 10^{-3} V_{OV}^2$$

$$V_{OV} = 0.354 \text{ V} \quad \rightarrow \quad V_{SG} = V_{OV} + |V_t| = 1.35 \text{ V}$$

$$V_{SG} = V_S - V_G \quad \rightarrow \quad V_G = 6 - 1.35 = 4.65 \text{ V}$$
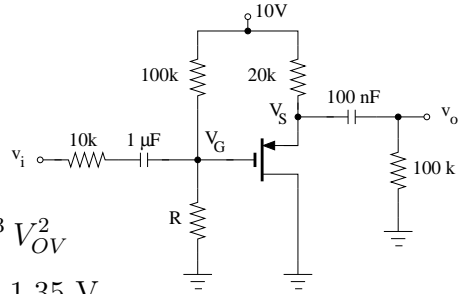
$$V_G = 4.65 = \frac{R}{R + 100 \text{ k}} \times 10 \quad \rightarrow \quad R = 87 \text{ k}$$



This is a common drain amplifier (source follower):

$$g_m = \frac{2I_D}{V_{OV}} = 1.13 \text{ mA/V} \quad r_o \rightarrow \infty$$

$$\frac{v_o}{v_g} = A_v = \frac{g_m(R_S \parallel R_L)}{1 + g_m(R_S \parallel R_L)}$$


$$R_S \parallel R_L = 20 \text{ k} \parallel 100 \text{ k} = 16.7 \text{ k}$$

$$\frac{v_o}{v_g} = \frac{1.13 \times 16.7}{1 + 1.13 \times 16.7} = 0.95$$

$$R_i = R \parallel 100 \text{ k} = 87 \text{ k} \parallel 100 \text{ k} = 46.5 \text{ k}$$

$$\frac{v_g}{v_i} = \frac{R_i}{R_i + 10 \text{ k}} = 0.82$$
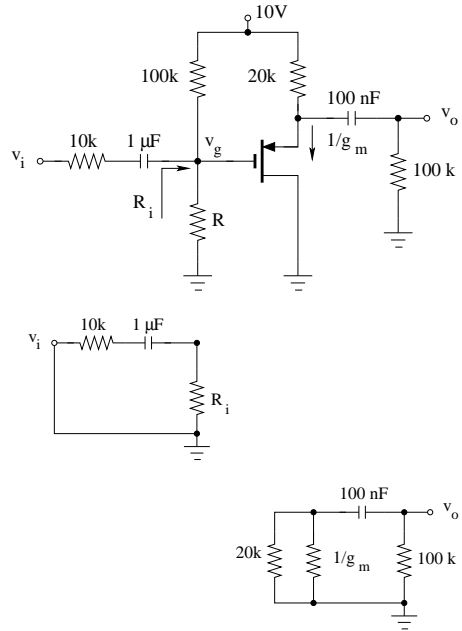
$$\frac{v_o}{v_i} = \frac{v_o}{v_g} \times \frac{v_g}{v_i} = (0.95)(0.82) = 0.78$$




To find f_L , we compute resistances seen across the terminals of the two capacitors (see circuits with $1/g_m \parallel 20 \text{ k} = 885 \parallel 20 \text{ k} = 850 \text{ } \Omega$)

$$f_{p1} = \frac{1}{2\pi(10 \text{ k} + R_i) \times 10^{-6}} = 2.82 \text{ Hz}$$

$$f_{p2} = \frac{1}{2\pi(100 \text{ k} + 850) \times 100 \times 10^{-9}} = 15.9 \text{ Hz}$$

$$f_L = f_{p1} + f_{p2} = 18.7 \text{ Hz}$$

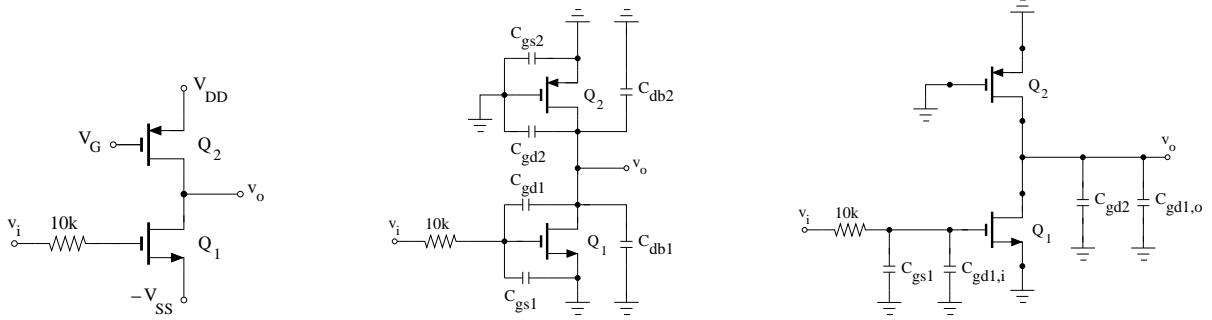Problem 5. Find f_H in the circuit below with identical transistors. Use $V_{OV} = 0.5$ V, $I_D = 50$ μ A, $V_A = 10$ V, $C_{gs} = 250$ fF, $C_{gd} = 80$ fF, and ignore C_{db} . (10 pts).



Including internal capacitances of transistors (middle circuit above with C_{db} also shown), we see that both C_{gs2} terminals are connected to the ground, C_{gd2} is between output and the ground, C_{gs1} is between input and the ground and C_{gd1} is between input and output. Using Miller's Theorem to replace C_{gd1} we arrive at the circuit above, right. Combining capacitors, we get:

$$g_{m1} = g_{m2} = \frac{2I_D}{V_{OV}} = 0.2 \text{ mA/V}$$

$$r_{o1} = r_{o2} = \frac{V_A}{I_D} = 200 \text{ k}$$

$$A = \frac{v_{d1}}{v_{g1}} = -g_{m1}(r_{o1} \parallel r_{o2}) = -g_{m1}(200 \text{ k} \parallel 200 \text{ k})$$


$$A = -0.2 \times 10^{-3} \times 100 \times 10^3 = -20$$

$$C_{gd1,i} = C_{gd1}(1 - A) = 80(1 + 20) = 1,680 \text{ fF}$$

$$C_{gd1,o} = C_{gd1}(1 - 1/A) = 80(1 + 1/20) = 84 \text{ fF}$$

$$C_{in} = C_{gd1,i} + C_{gs1} = 1,680 + 250 = 1,930 \text{ fF}$$
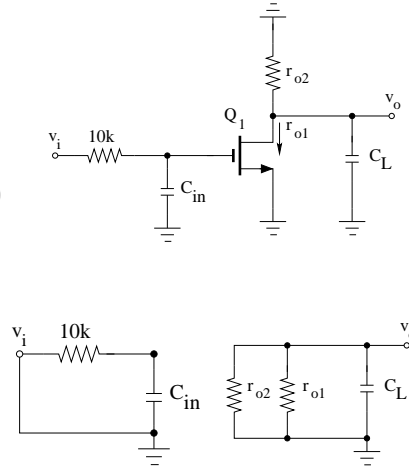
$$C_L = C_{gd1,o} + C_{gd2} = 84 + 80 = 164 \text{ fF}$$



Computing the time constants associated with each capacitor (see circuits above):

$$\tau_{in} = 10^4 C_{in} = 10^4 \times 1,930^{-15} = 1.93 \times 10^{-8}$$

$$\tau_L = (r_{o1} \parallel r_{o2}) C_L = 100 \times 10^3 \times 164^{-15} = 1.64 \times 10^{-8}$$

$$\tau = \tau_{in} + \tau_L = 3.57 \times 10^{-8}$$

$$f_H = 1/(2\pi\tau) = 4.4 \text{ MHz}$$

Problem 6. Consider the circuit below with identical transistors having $V_{OV} = 0.5$ V and $V_A = 10$ V. Drain current of Q5 is $200 \mu\text{A}$. Find the differential gain for A) $R_p = 0$, and B) $R_p = 1$ k.

Because of symmetry, the drain current of Q5 is equally divided between the two half-circuits:

$$I_{D1} = I_{D2} = I_{D3} = I_{D4} = 100 \mu\text{A}$$

$$g_{m1} = g_{m2} = g_{m3} = g_{m4} = \frac{2I_D}{V_{OV}} = 0.4 \text{ mA/V}$$

$$r_{o1} = r_{o2} = r_{o3} = r_{o4} = \frac{V_A}{I_D} = 100 \text{ k}$$

Part A, $R_p = 0$: Using half circuit concept, we arrive at a CS amplifier (Q1) with Q3 acting as its active load:




$$\frac{v_{o1}}{-0.5v_d} = -g_{m1}(r_{o1} \parallel r_{o3})$$

$$\frac{v_{o1}}{-0.5v_d} = -g_{m1}(100 \text{ k} \parallel 100 \text{ k})$$

$$\frac{v_{o1}}{-0.5v_d} = -0.4 \times 10^{-3} \times 50 \times 10^3 = -20$$

$$v_{o1} = -10(-0.5v_d) = 10v_d$$
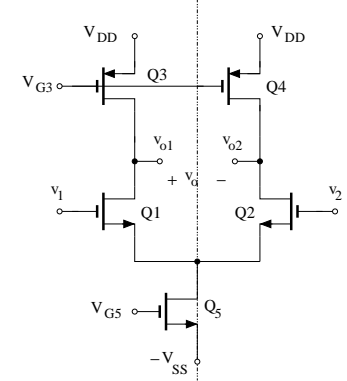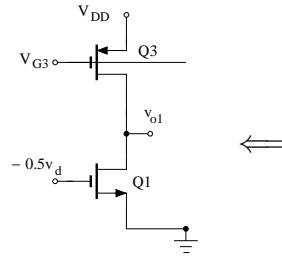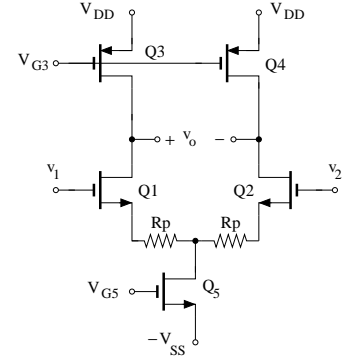
$$v_{o2} = -v_{o1} = -10v_d \quad \longrightarrow v_o = v_{o1} - v_{o2} = -20v_d$$



$$\longrightarrow A_d = v_o/v_d = -20$$



Part B, $R_p = 1$ k: Using half circuit concept, we arrive at a CS amplifier with source resistance (Q1) with Q3 acting as its active load:

$$\frac{v_{o1}}{-0.5v_d} = -\frac{g_{m1}r_{o3}}{1 + g_{m1}R_p + r_{o3}/r_{o1}}$$

$$\frac{v_{o1}}{-0.5v_d} = -\frac{0.4 \times 10^{-3} \times 10^5}{2 + 0.4 \times 10^{-3} \times 1 \times 10^3} = -16.7$$

$$v_{o1} = -10(-0.5v_d) = 8.3v_d$$
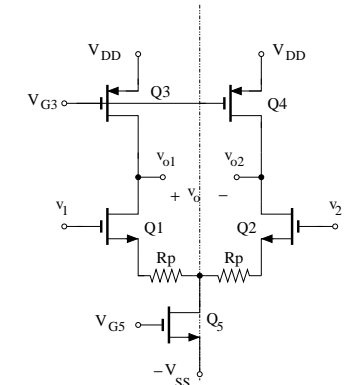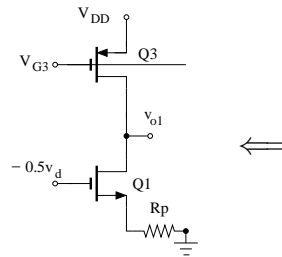
$$v_{o2} = -v_{o1} = -8.3v_d \quad \longrightarrow v_o = v_{o1} - v_{o2} = -16.7v_d$$



$$\longrightarrow A_d = v_o/v_d = -16.7$$