



IMPORTANT: Besides your **calculator** and the sheets you use for calculations you are only allowed to have an A4 sized “**copy sheet**” during this exam. Notes, problems and alike are not permitted. **Please submit your “copy sheet” along with your solutions.** You may get your “copy sheet” back after your solutions have been graded.

EHB222E INTRODUCTION TO ELECTRONICS (12137)

Final Exam 8 January 2017 12-14



Bora DÖKEN, Bülent YAĞCI, İbrahim ÇATALKAYA, İnci ÇİLESİZ

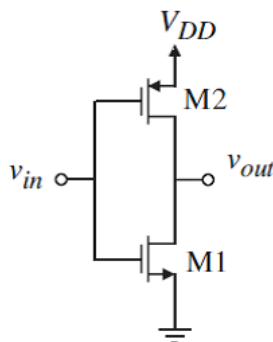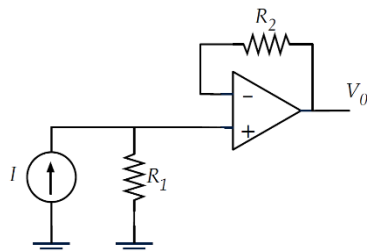1. Consider the op-amp circuit shown on the right. Determine the current I_x and output voltage V_A when $V_1 = 1V$ and $V_2 = 2V$. (12.5 points)
2. Consider the op-amp circuit shown below left. Calculate the output voltage. ($R_1 = R_2 = 2k\Omega$, $I = 1mA$) (12.5 points)



3. For the transistors shown below $\beta = h_{fe} = h_{FE} = 200$, $V_{BE} = 0.6V$, and $V_T = 25mV$. All capacitors are ideal.

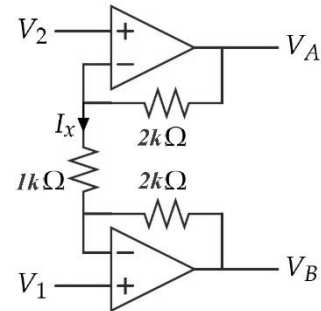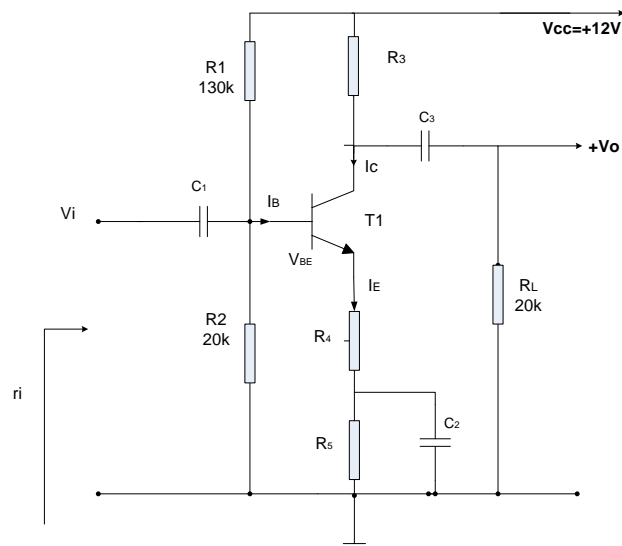- a) Find R_3 , R_4 and R_5 for $I_C = 1mA$, $V_{CE} = 4V$ and $r_i = 10k\Omega$ (12.5 points)
- b) Calculate v_o/v_i . (12.5 points).



4. Find the gain and output resistance of the CMOS amplifier shown above left. You need to draw the small signal circuit (not neglecting V_A) to analyze this circuit. (20 points)
5. When a transistor amplifier is operating, the current in any branch is
 - a) Sum of a.c. and d.c. b) a.c. only c) d.c. only d) difference of a.c. and d.c. e) none of the above
6. The purpose of capacitors in a transistor amplifier is to
7. In the d.c. equivalent circuit of a transistor amplifier, the capacitors are considered
8. Operating point of a transistor amplifier represents
 - a) Values of I_C and V_{CE} when signal is applied
 - b) The magnitude of signal
 - c) Zero signal values of I_C and V_{CE}
 - d) Gain of the amplifier
 - e) None of the above
9. In a p-channel MOSFET, the charge carriers are
10. In the breakdown region, a Zener diode behaves like a source.
11. What is a semiconductor? How does a semiconductor differ from a conductor? Explain within two sentences.
12. What are some of the similarities and differences between MOSFET and BJT transistors. Provide at least 2 of each.

GOOD LUCK

Problem 1: $I_x = 1 \text{ mA}$, $V_A = 4 \text{ V}$


Problem 2: $V_{+} = 2 \text{ V}$ Therefore $V_o = 2 \text{ V}$ because there is no current flow.

Problem 3:

$$\begin{aligned}
 V_{BB} &= \frac{R_2 \cdot V_{CC}}{R_1 + R_2} = 1.6 \text{ V} & R_{BB} &= R_1 \parallel R_2 = 17.3 \text{ k} \\
 I_C &\approx I_E = h_{FE} \cdot \frac{V_{BB} - V_{BE}}{R_{BB} + (h_{FE} + 1) R_E} \Rightarrow R_E = 0.91 \text{ k} \\
 & & R_E &= R_4 + R_5 \\
 r_i &= R_1 \parallel R_2 \parallel r_i' & r_i' &= 23.7 \text{ k} \\
 r_i' &= h_{FE}(r_e + R_E) & R_E &= R_4 & \frac{V_T}{I_E} = r_e = 25 \Omega \\
 R_E &= R_4 = 93.5 \Omega & R_5 + R_4 &= 910 \Omega \\
 & & R_5 &= 816.5 \Omega \\
 V_{CC} &= I_C \cdot R_3 + V_{CE} + R_E \cdot I_E \Rightarrow R_C = 7.1 \text{ k} = R_3 \\
 & & R_C' &= R_3 \parallel R_L = 5.2 \text{ k} \\
 \frac{V_o}{V_i} &= - \frac{R_C'}{r_e + R_E} = - \frac{5.2 \text{ k}}{25 + 93.5} = -44
 \end{aligned}$$

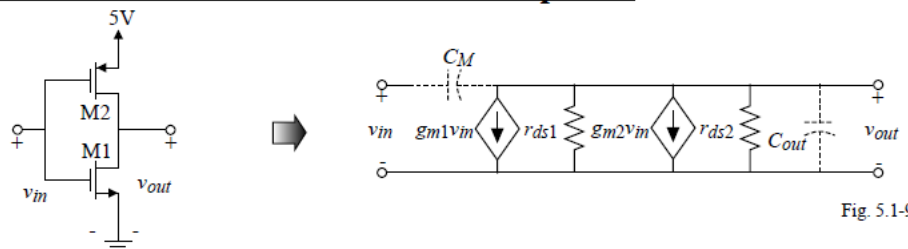Problem 4: [http://www.yildiz.edu.tr/~nicoskun/Chap05\(7_5_06\).pdf](http://www.yildiz.edu.tr/~nicoskun/Chap05(7_5_06).pdf)

Small-Signal Performance of the Push-Pull Amplifier



Small-signal analysis gives the following results:

$$\begin{aligned}
 \frac{v_{out}}{v_{in}} &= \frac{-(g_{m1} + g_{m2})}{g_{ds1} + g_{ds2}} = -\sqrt{(2/I_D)} \left[\frac{\sqrt{K'_N(W_1/L_1)} + \sqrt{K'_P(W_2/L_2)}}{\lambda_1 + \lambda_2} \right] \\
 R_{out} &= \frac{1}{g_{ds1} + g_{ds2}}
 \end{aligned}$$

5. When a transistor amplifier is operating, the current in any branch is
 - a) Sum of a.c. and d.c.
 - b) a.c. only
 - c) d.c. only
 - d) difference of a.c. and d.c.
 - e) none of the above
6. The purpose of capacitors in a transistor amplifier is to couple or bypass a.c. component
7. In the d.c. equivalent circuit of a transistor amplifier, the capacitors are considered open
8. Operating point of a transistor amplifier represents
 - a) Values of I_C and V_{CE} when signal is applied
 - b) The magnitude of signal
 - c) Zero signal values of I_C and V_{CE}
 - d) Gain of the amplifier
 - e) None of the above
9. In a p-channel MOSFET, the charge carriers are holes
10. In the breakdown region, a Zener diode behaves like a constant voltage source.
11. What is a semiconductor? How does a semiconductor differ from a conductor? Explain within two sentences.
12. What are some of the similarities and differences between MOSFET and BJT transistors. Provide at least 2 of each.