

**EE232-INTRODUCTION TO ELECTRONICS**  
**EXERCISE-2.2**

**E2.2** Design a voltage amplifier with a gain of -10 and an input resistance of 10kΩ by using an operational amplifier.

**S2.2** Having learned the inverting amplifier configuration, we can easily solve this question. Consider the circuit given in Figure-1 below,

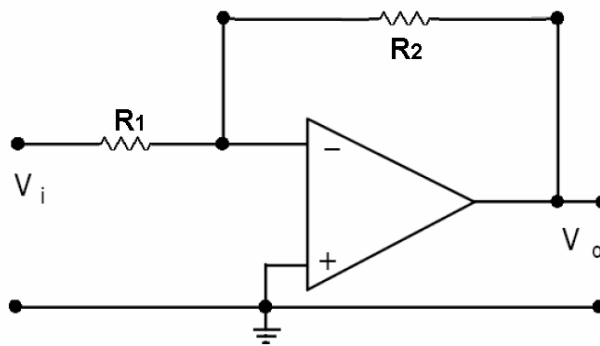


Figure-1

We know that the gain of this circuit is equal to

$$A_V = \frac{V_o}{V_i} = -\frac{R_2}{R_1} \quad (1)$$

In order to obtain the gain of -10, we need the condition of

$$-\frac{R_2}{R_1} = -10 \Rightarrow R_2 = 10R_1 \quad (2)$$

Now, we should provide the second design condition, that is, the input resistance. The input resistance is equal to the ratio of the input voltage to the input current ( $V_i/i_i$ ). Since the opamp is used in the closed-loop configuration with a negative feedback the inputs are equal to each other. Thus, as seen from the figure, the inverting input is virtually grounded. Therefore, the input voltage  $V_i$  is appeared completely across the resistor  $R_1$ . So, the input current is obtained as  $i_i = V_i/R_1$ , that is, the input resistance of the circuit is  $R_1$ . In order to obtain an input resistance of 10kΩ,  $R_1$  should be made 10kΩ. Then, from Equation-2,  $R_2$  is obtained as 100kΩ.

$$R_1 = 10\text{k}\Omega$$

$$R_2 = 100\text{k}\Omega$$