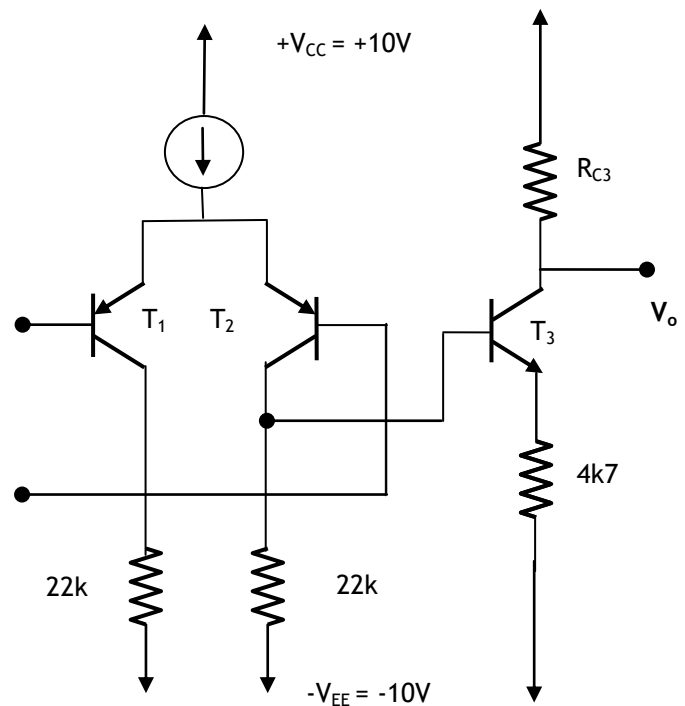


**IMPORTANT:** Besides your **calculator** and the sheets you use for calculations you are only allowed to have an A4 sized “**copy sheet**” during this exam. Notes, problems and alike are not permitted. **Please submit your “copy sheet” along with your solutions.** You may get your “copy sheet” back after your solutions have been graded. **Do not forget to write down units and convert units carefully! Cell phones are not allowed and should be placed on the front desk before the exam.**

**EHB222E INTRODUCTION TO ELECTRONICS (12137)**  
**Midterm Exam #2** ✎ **5 December 2017** ⌚ **15.30-17.30**  
**İnci ÇİLESİZ, PhD, Ensar VAHAPOĞLU**  
**EEF 5302-5202**


1. Study the 2-stage BJT amplifier circuit shown on the left with  $V_T = 25$  mV,  $|V_{BE}| = 0,6$  V,  $h_{FE} = 200$  for all three transistors. Do NOT forget  $h_{oe} = h_{re} = 0$

- Design a current source that will provide 0,4 mA biasing current to the differential stage. (10 points)
- Choose  $R_{C3}$  such that the such that, waveform distortion at the output  $V_o$  is minimum and symmetrical. Do NOT neglect base currents. (10 points)
- Find the small signal voltage gain of the 2-stage amplifier and the CMRR. (20 points)
- Calculate the input and output resistances. (10 points)



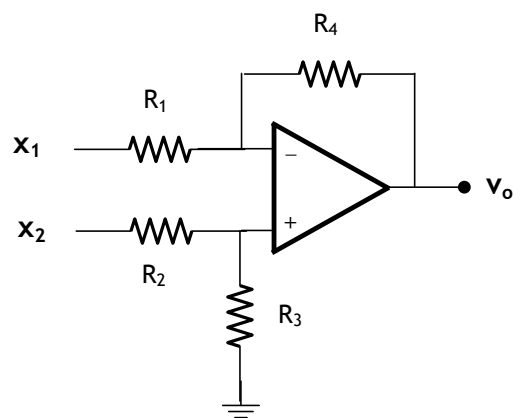2. Analysis/synthesis:

- Analyze the OPAMP circuit shown on below right and express  $v_o$  in terms of the resistors  $R_1, \dots, R_4$ , and inputs  $x_1$  and  $x_2$ . (25 points)
- Taking advantage of the analysis above, design an OPAMP circuit that will realize the function  $v_o = 3x_3 - 2x_2 - 5x_1$ . Please use meaningful resistor values. (25 points)



**BONUS:** Who gave these units their names and which country are they from: mV, kW, dB, K. **Each correct answer 2,5 points! Wrong answers -2,5 each!!!!**


**GOOD LUCK**

## SOLUTIONS

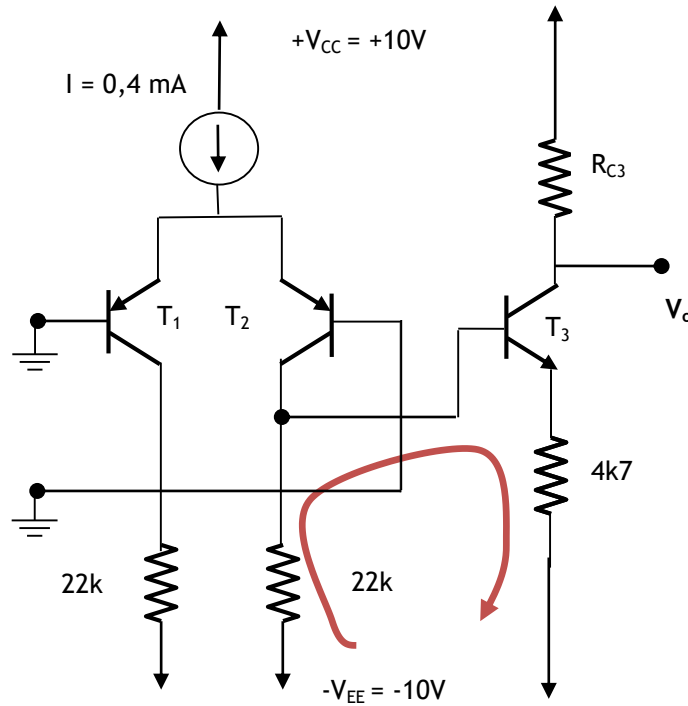1. This circuit has to be analyzed in parts. You can easily design the current mirror. So this part is left to you like before. **If you have trouble check solutions to MT1 of Spring 2011.**

Without neglecting the base currents of the differential (the very first) stage, for  $V_i = 0$  V

$$I_{C1} = I_{C2} = \frac{h_{FE}}{h_{FE} + 1} \cdot \frac{I_{ref}}{2} = \frac{200}{200 + 1} \cdot \frac{0,4mA}{2} \Rightarrow I_{C1} = I_{C2} = \underline{\underline{0,199mA}}$$



Following the brown loop  $-(I_{C2} - I_{B3})22k + V_{BE3} + (h_{FE} + 1)I_{B3}4k7 = 0$

$$I_{C3} = h_{FE} \frac{22k * I_{C2} - V_{BE3}}{(h_{FE} + 1)4k7 + 22k} = 200 \frac{22k * 0,199mA - 0,6V}{(200 + 1)4k7 + 22k} = \underline{\underline{0,782mA}}$$

for waveform distortion at the output  $V_o$  to be minimum and symmetrical:

$$V_o = 0V \Rightarrow I_{C3}R_{C3} = V_{CC} = 10V \Rightarrow R_{C3} = \frac{V_{CC} - V_o}{I_{C3}} = \frac{10V}{0,782mA} = \underline{\underline{12k8}}$$

$$\frac{v_o}{v_i} = \frac{v_o}{v_{b3}} \cdot \frac{v_{b3}}{v_i} = -\frac{R_{C3}}{r_{e3} + R_{e3}} \cdot \frac{22k \parallel r_{i3}}{2r_{e1/2}} \text{ with}$$

$$\begin{cases} r_{e3} = \frac{V_T}{I_{C3}} = \frac{25mV}{0,782mA} = \underline{\underline{32\Omega}} \\ r_{e1/2} = \frac{V_T}{I_{C1/2}} = \frac{25mV}{0,199mA} = \underline{\underline{125,6\Omega}} \\ r_{i3} = h_{fe}(r_{e3} + R_{e3}) = 200(32 + 4k7) = \underline{\underline{946k}} \end{cases}$$

$$\frac{v_o}{v_i} = -\frac{R_{C3}}{r_{e3} + R_{e3}} \cdot \frac{22k \parallel r_{i3}}{2r_{e1/2}} = -\frac{12k8}{32 + 4k7} \cdot \frac{22k \parallel 966k2}{2 \cdot 125,6} = \underline{\underline{-231,5}}$$

$$CMRR = 20 \log_{10} \left| \frac{A_d}{A_c} \right| = 20 \log_{10} \left| \frac{2R_{E1/2} + r_{e1/2}}{r_{e1/2}} \right| \text{ since there is no resistor connected to the common emitters of the differential stage, } R_{E1/2} \rightarrow \infty \Rightarrow CMRR \rightarrow \infty$$

As the 2<sup>nd</sup> stage is a common emitter circuit  $r_o = R_{C3} = \underline{\underline{12k8}}$

$$r_i = r_{i1/2} = 2h_{fe}r_{e1/2} = \underline{\underline{20k250}}$$

2. The function realized by the given circuit is found from solving


$$\frac{x_1 - v_-}{R_1} = \frac{v_- - v_o}{R_4} \text{ where } v_- = v_+ = \frac{R_3}{R_2 + R_3} x_2$$

$$\Rightarrow v_o = -\frac{R_4}{R_1} x_1 + \frac{R_3}{R_2 + R_3} \cdot \left( 1 + \frac{R_4}{R_1} \right) x_2$$

For example, if  $\frac{R_4}{R_1} = \frac{4k}{1k} = 4$ ;  $\frac{R_3}{R_2 + R_3} = \frac{2k}{2k + 3k} = \frac{2}{5}$  then the circuit realizes the function

$$v_o = 2x_2 - 4x_1$$

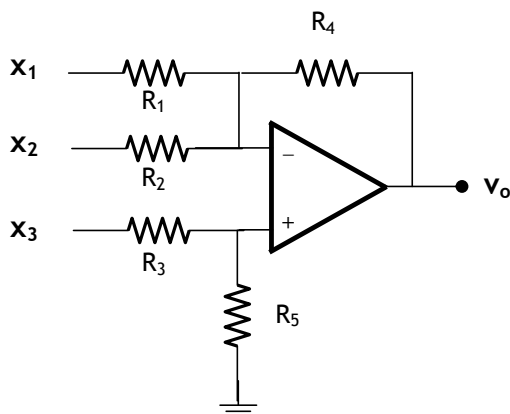In a similar way  $v_o = 3x_3 - 2x_2 - 5x_1$  can be realized by the OPAMP circuit below:



Now we have to find the R values

$$\frac{R_4}{R_1} = 5 \Rightarrow \underline{\underline{R_4 = 10k}}, \underline{\underline{R_1 = 2k}}; \frac{R_4}{R_2} = 2 \Rightarrow \underline{\underline{R_2 = 5k}}$$

$$\frac{R_5}{R_3 + R_5} \left( 1 + \frac{R_4}{R_1} + \frac{R_4}{R_2} \right) = \frac{R_5}{R_3 + R_5} (1 + 5 + 2) = 3 \Rightarrow \frac{R_5}{R_3 + R_5} = \frac{3}{8} \Rightarrow \underline{\underline{R_5 = 3k}}, \underline{\underline{R_3 = 5k}}$$