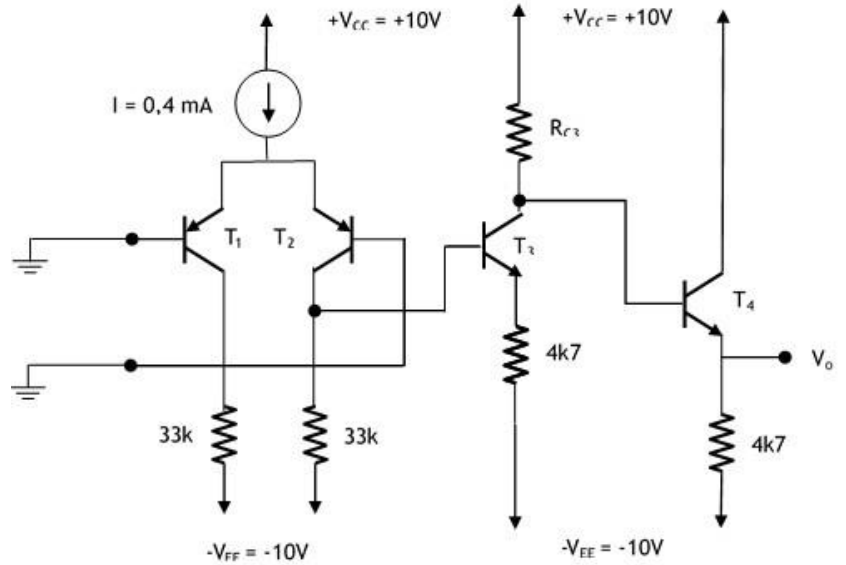



**IMPORTANT:** Besides your **calculator** and the sheets you use for calculations you are only allowed to have an A4 sized “**copy sheet**” during this exam. Notes, problems and alike are not permitted. **Please submit your “copy sheet” along with your solutions.** You may get your “copy sheet” back after your solutions have been graded. **Do not forget to write down units and convert units carefully! Cell phones are not allowed and should be placed on the front desk before the exam.**

**EEB222E INTRODUCTION TO ELECTRONICS (11394)**  
**Midterm Exam #2** ✎ **8 December 2015** ⌚ **13.30-15.30**  
**İnci ÇİLESİZ, PhD, Hacer ATAR YILDIZ, PhD**  
**EEF 4104**

1. You know the 3-stage BJT amplifier circuit from your first exam. Analyze the circuit at DC and AC with  $|V_{BE}| = 0,6 \text{ V}$ ,  $h_{FE} = h_{fe} = 200$  for all four transistors. **Do not neglect base currents.**
  - a. Design a current source that will provide **0,4 mA** biasing current to the differential stage. (10)
  - b. Choose  $R_{C3}$  such that,  $T_3$  is in active mode (10)
  - c. Find the gain  $v_o/v_i$ , input and output resistances with  $V_T = 25 \text{ mV}$ . (20)



2. Analyze the 3-stage amplifier circuit below right. For all transistors  $h_{FE} = h_{fe} = 100$ ,  $V_T = 25 \text{ mV}$ ,  $|V_{BE}| = 0,6 \text{ V}$ ,  $h_{oe} = h_{re} = 0$ .
  - a. Find the collector currents of all 4 transistors and value of  $R_{C3}$ , such that, waveform distortion at the output  $v_o$  is minimum and symmetrical. (20)
  - b. Calculate the total voltage gain, input and output resistance of the 3-stage BJT amplifier. Also calculate CMRR of the first stage. (40) If you could not find collector currents and  $R_{C3}$  in (a), you may assume  $I_{C1} = I_{C2} = I_{C3} = I_{C4} = 1 \text{ mA}$  and  $R_{C3} = 10\text{k}$ .

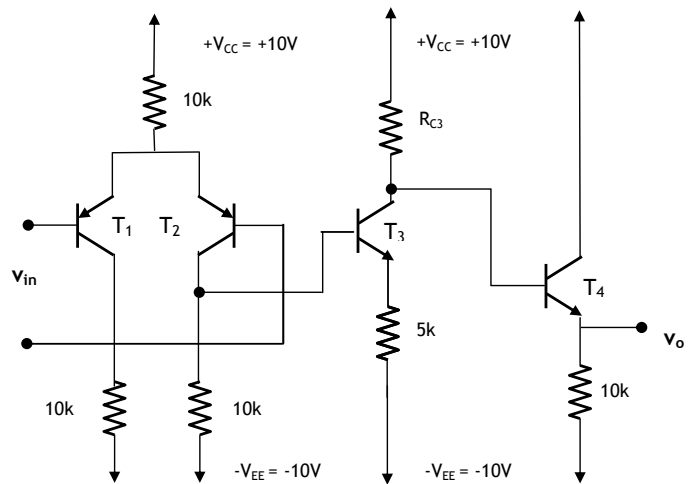

**GOOD LUCK**

**SOLUTIONS:**

1. DC characteristics are to be studied.

a. You do your own design!

b. Without neglecting the base currents of the differential (the very first) stage, for  $V_i = 0$  V

$$I_{C1} = I_{C2} = \frac{h_{FE}}{h_{FE} + 1} \cdot \frac{I_{ref}}{2} = \frac{200}{200 + 1} \cdot \frac{0,4mA}{2} \Rightarrow I_{C1} = I_{C2} = \underline{\underline{0,199mA}}$$

$$-(I_{C2} - I_{B3})33k + V_{BE3} + (h_{FE} + 1)I_{B3}4k7 = 0$$

$$I_{C3} = h_{FE} \frac{33k * I_{C2} - V_{BE3}}{(h_{FE} + 1)4k7 + 33k} = 200 \frac{33k * 0,199mA - 0,6V}{(200 + 1)4k7 + 33k} = \underline{\underline{1,2mA}}$$

$$\text{Now we need to find the base voltage of } T_3. V_{B3} = -10V + (I_{C2} - I_{B3})33k = \underline{\underline{-3,63V}}$$

For  $T_3$  to be in active mode  $V_{B3} \leq V_{C3}$ . I take  $V_{C3} = -3,5V > -3,63V$ . Thus

$$V_{C3} = V_{B4} = -10V + 4k7 \cdot I_{E4} + V_{BE4} = -10V + 4k7 \cdot I_{B4}(h_{FE} + 1) + 0,6V = -3,5V$$

$$\Rightarrow I_{C4} = h_{FE} \cdot I_{B4} = h_{FE} \frac{10V - 3,5V - 0,6V}{4k7 \cdot (h_{FE} + 1)} = \underline{\underline{1,0mA}}$$

For  $T_3$  to be in active mode

$$V_{C3} = -3,5V = 10V - R_{C3}(I_{C3} + I_{B4}) \Rightarrow R_{C3} \leq \frac{10V + 3,5V}{(I_{C3} + I_{B4})} = \underline{\underline{11k1}}$$

AC Analysis: Let's first calculate the AC resistances

$$r_{e1} = r_{e2} = \frac{V_T}{I_{C1}} = \underline{\underline{125,6\Omega}}; r_{e3} = \frac{V_T}{I_{C3}} = \underline{\underline{20,5\Omega}}; r_{e4} = \frac{V_T}{I_{C4}} = \underline{\underline{25,1\Omega}}$$

$$\text{Now the gain is } \frac{v_o}{v_i} = \frac{v_o}{v_{b3}} \cdot \frac{v_{b4}}{v_{b3}} \cdot \frac{v_{b3}}{v_i} = \frac{4k7}{4k7 + r_{e4}} \cdot \frac{-R_{C3} \parallel r_{i4}}{4k7 + r_{e3}} \cdot \frac{33k \parallel r_{i3}}{2r_{e1/2}} \text{ with}$$

$$r_i = r_{i1/2} = 2h_{fe}r_{e1/2} = 2 \cdot 200 \cdot \frac{25mV}{0,199mA} = \underline{\underline{50k25}};$$

$$r_{i3} = h_{fe}(r_{e3} + 4k7) = 944k$$

$$r_{i4} = h_{fe}(r_{e4} + 10k) = 945k$$

$$\text{Resulting in } \frac{v_o}{v_i} = \frac{4k7}{4k7 + r_{e4}} \cdot \frac{-11k11 \parallel r_{i4}}{4k7 + r_{e3}} \cdot \frac{33k \parallel r_{i3}}{2r_{e1/2}} = 0,994 \cdot (-2,36) \cdot 126,9 \cong \underline{\underline{-293,6}}$$

$$r_o = r_{o4} = R_{E4} \parallel \left[ r_{e4} + \frac{R_S}{h_{fe}} \right] = R_{E4} \parallel \left[ r_{e4} + \frac{r_{o3}}{h_{fe}} \right] = \underline{\underline{51\Omega}} \text{ where } r_{o3} = R_{C3} = \underline{\underline{5k35}}$$

2. DC characteristics are to be studied.

DC Analysis: The first stage of the 3-stage amplifier is a differential stage. Since both transistors are ideal, their collector currents are the same

$$I_{C1} = I_{C2} = \frac{h_{FE}}{h_{FE} + 1} \left[ \frac{V_{CC} - V_{BE1}}{2R_E} \right] = \frac{100}{101} \cdot \frac{10V + V_{BE1}}{20k} = \frac{100}{101} \cdot \frac{10V - 0,6V}{20k} \cong \underline{\underline{0,47mA}}$$

Now, following the blue loop

$$-(I_{C2} - I_{B3})10k + V_{BE3} + (h_{FE} + 1)I_{B3}5k = 0$$


$$I_{C3} = h_{FE} \frac{10k * I_{C2} - V_{BE3}}{(h_{FE} + 1)5k + 10k} = \underline{\underline{0,8mA}}$$

We are told that waveform distortion at the output  $V_o$  should be minimum and symmetrical. That means  $V_o = 0V$ .

$$I_{E4} = \frac{0V - (-V_{EE})}{10k} \text{ or}$$

$$(h_{FE4} + 1)I_{B4}10k = 10V$$
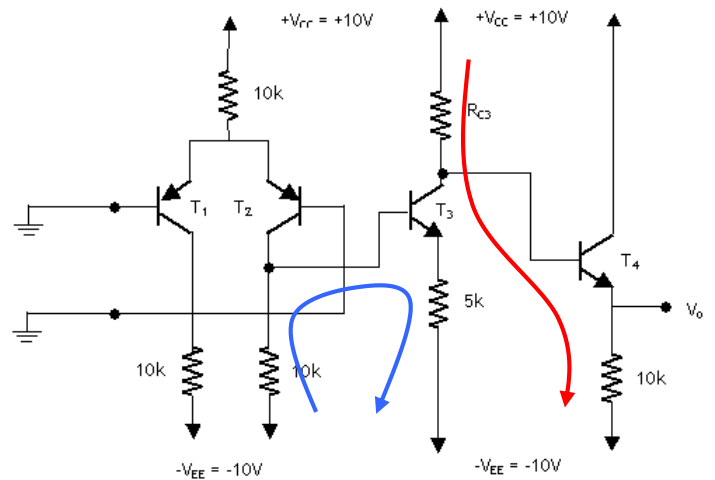
$$\Rightarrow I_{C4} = h_{FE4}I_{B4} = \underline{\underline{0,99mA}}$$



$$\text{Also, } V_{B4} = +V_{CC} - R_{C3} * (I_{C3} + I_{B4}) = +10V - R_{C3} * (0,91mA + 9,9\mu A) = V_{BE4} = 0,6V$$

$$\text{Therefore, } R_{C3} = \frac{10V - 0,6V}{0,8mA + 9,9\mu A} = \underline{\underline{11k6}}$$

AC Analysis: Let's first calculate the AC resistances

$$r_{e1} = r_{e2} = \frac{V_T}{I_{C1}} = \frac{25mV}{0,47mA} = \underline{\underline{53,2\Omega}}; r_{e3} = \frac{V_T}{I_{C3}} = \frac{25mV}{0,8mA} = \underline{\underline{31,25\Omega}}; r_{e4} = \frac{V_T}{I_{C4}} = \frac{25mV}{0,99mA} = \underline{\underline{25,25\Omega}}$$

$$A_v = \frac{v_o}{v_{in}} = \frac{v_o}{v_{b4}} \cdot \frac{v_{b4}}{v_{b3}} \cdot \frac{v_{b3}}{v_{in}} = + \frac{R_{e4}}{r_{e4} + R_{e4}} \cdot \left[ - \frac{R_{C3} \parallel r_{i4}}{r_{e3} + R_{e3}} \right] \cdot \left[ + \frac{R_{C2} \parallel r_{i3}}{2r_{e1}} \right]$$

$$r_{i3} = h_{fe}(r_{e3} + R_{e3}) = 100(31,25 + 5k) = \underline{\underline{503k}}$$

$$r_{i4} = h_{fe}(r_{e4} + R_{e4}) = 100(25,25 + 10k) = \underline{\underline{1M}}$$

$$\Rightarrow A_v = \frac{10k}{25,25 + 10k} \cdot \left[ - \frac{11k6 \parallel 1M}{31,25 + 5k} \right] \cdot \left[ \frac{10k \parallel 503k}{2 * 53,2} \right] = 0,997 * (-2,279) * 92,167 \cong \underline{\underline{-209,5}}$$

$$r_o = r_{o4} = R_{E4} \parallel \left[ r_{e4} + \frac{R_S}{h_{fe}} \right] = R_{E4} \parallel \left[ r_{e4} + \frac{r_{o3}}{h_{fe}} \right] = \underline{\underline{139\Omega}} \text{ where } r_{o3} = R_{C3} = \underline{\underline{11k6}}$$

$$CMRR = 20 \log_{10} \left| \frac{2R_E + r_{e1/2}}{r_{e1/2}} \right| = 20 \log_{10} \left| \frac{2 \cdot 10k + 53,2\Omega}{53,2\Omega} \right| = \underline{\underline{51,5dB}}$$