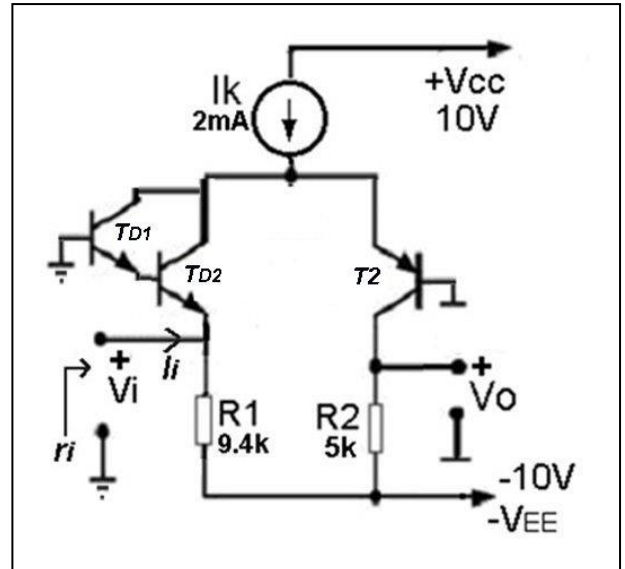


P1 For the transistors in the figure, $\beta_F=200$, $|V_{BE}|=0.6V$, $V_T=25mV$, $V_A=\infty$. **TD and T2 have the same collector current value in DC case.**

a) In ac case, find the input current value ($i_i=?$) for the input voltage value $V_i=10mV$.

b) Design a current mirror structure in place of the current source $I_k=2mA$.
(You can use the same transistors)



P2- For the MOS transistors in the Figure, $\beta_1=\beta_2=\beta_3=0.4mA/V^2$, $\beta_4=\beta_5=0.8mA/V^2$ and $|V_{TH1}|=|V_{TH2}|=V_{TH3}=V_{TH4}=V_{TH5}=0.5V$ are given.

a) Find I_{DQ4} for $V_{in}=0$ in DC case.

b) Find i_{d3}/V_{in} (ac trans-conductance gain between gate1 and drain3).

c) Find ac gain (V_{out}/V_{in}) of the circuit.

