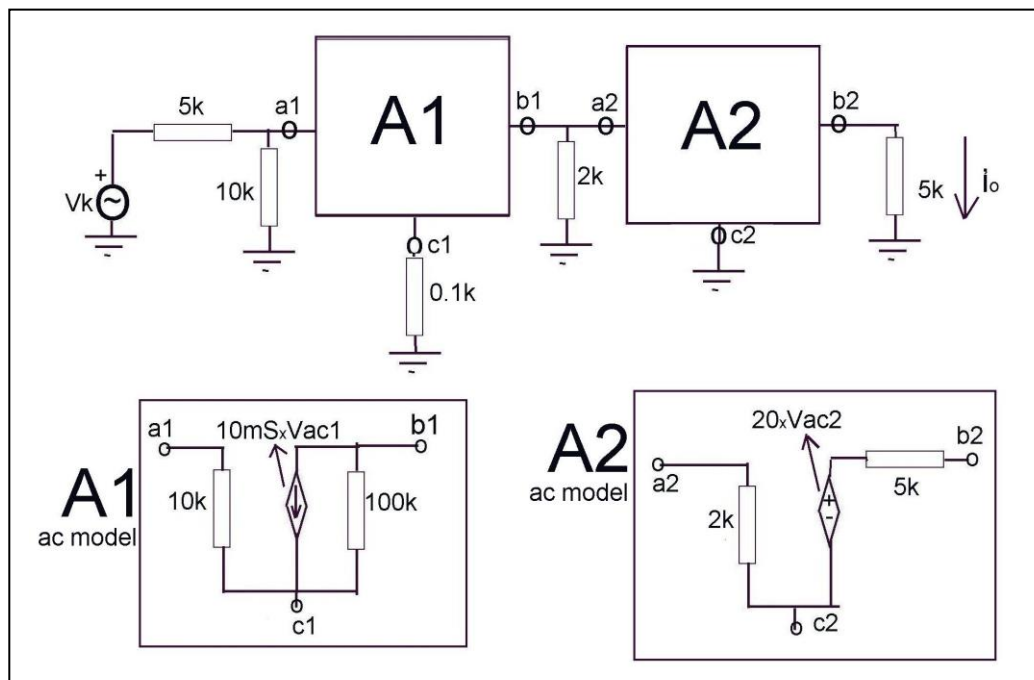


Final exam includes 5 problems.

Write your answers on A4-white papers and sign each page.



P1 ac case of an amplifier circuit including two amplifiers (A1 and A2) is shown in the picture, above. The ac models of A1 and A2 are given in the picture, below. Find the ac transconductance gain of the circuit ($G_m = i_o / v_k$). (15P)


P2 For the MOSFETs in the figure, $k_p' = \mu_p c_{ox} = 40 \mu A/V^2$, $k_n' = \mu_n c_{ox} = 100 \mu A/V^2$, $V_{An} = V_{Ap} = 40V$, $V_{Th,p} = -0.5V$, $V_{Th,n} = 0.5V$ are given.

$I_o = 1mA$, $(W/L)_N = 20$, $\beta_N = \beta_P$ are given.

a) Find V_{GGN} and V_{GGP} . (10P)

b) Find ac differential gain of the circuit $v_o / (v_{i1} - v_{i2})$. (10P)

c) Find CMRR of the circuit. (10P)

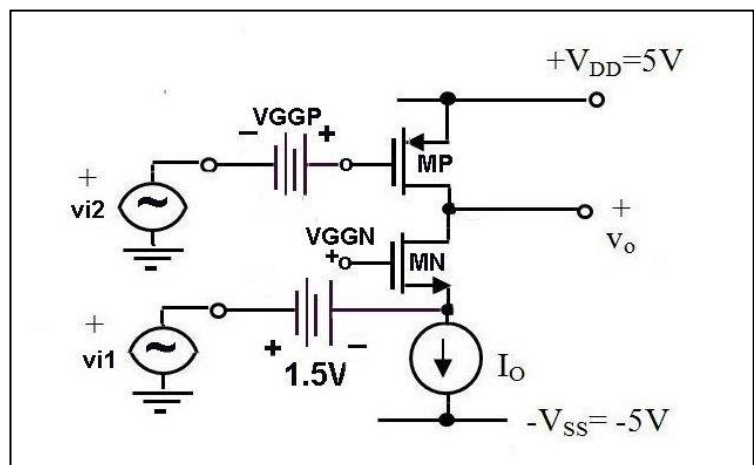


P3 For the MOSFET in the figure, $\beta=4\text{mA/V}^2$ and $V_{Th}=1\text{V}$ are given. the OPAMP is **ideal**.
The bias point for the input is given as $V_{iDC}=0\text{V}$.


a) Find ac gain of the circuit (V_o/V_i). (10P)

b) Find the maximum V_i value for the amplifier application. (10P)

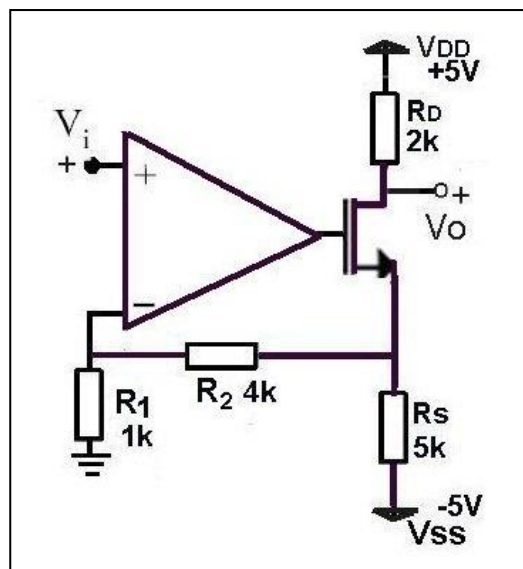b) Find the minimum V_i value for the amplifier application. (10P)



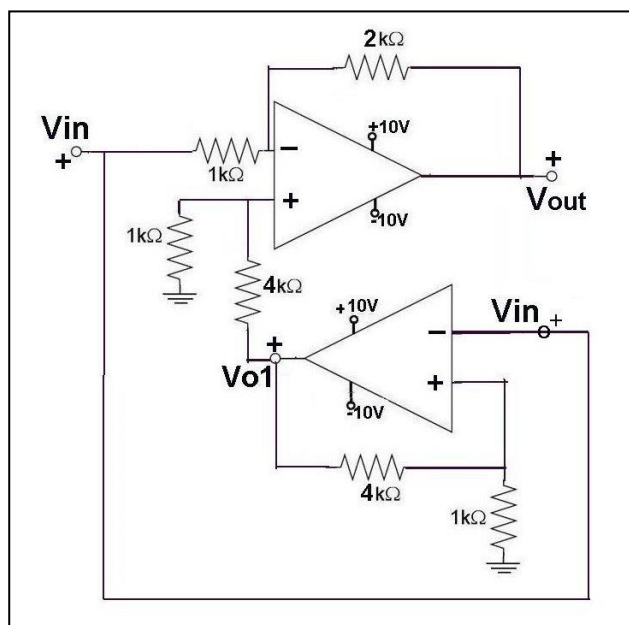P4 Draw the transfer characteristic of the circuit given in the figure ($V_{out}-V_{in}$). (15P)



P5 Draw the transfer characteristic of the circuit given in the figure ($V_{out}-V_{in}$). (15P)

