


IMPORTANT: Besides your **calculator** and the sheets you use for calculations you are only allowed to have an A4 sized “**copy sheet**” during this exam. Notes, problems and alike are not permitted. **Please submit your “copy sheet” along with your solutions.** You may get your “copy sheet” back after your solutions have been graded. **Do not forget to write down units and convert units carefully! Cell phones are not allowed and should be placed on the front desk before the exam.**

EHB222E INTRODUCTION TO ELECTRONICS (12137)
Midterm Exam #1 ✎ **24 October 2017** ⌚ **17.00-19.00**
İnci ÇİLESİZ, PhD, Ensar VAHAPOĞLU
EEF 5302-5304

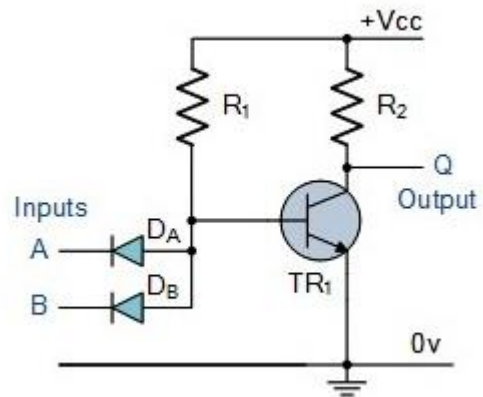1. Assume you are to create a diode using n- and p-typed doped silicon with the following doping parameters:
 $N_D = 5 \cdot 10^{15} / \text{cm}^3$, and $N_A = 10^{17} / \text{cm}^3$. (30 points)

- Find the barrier voltage and saturation current for a junction area of $0,1 \text{ mm}^2$. Calculate the specific conductivities of n- and p-type doped silicon.
- Determine the depletion zone width in unbiased state.
- Calculate the junction capacitance when this diode is reverse biased with 2 V.

$L_n = 10 \text{ } \mu\text{m}$, $L_p = 5 \text{ } \mu\text{m}$, $\mu_n = 1350 \text{ cm}^2/\text{Vs}$, $\mu_p = 480 \text{ cm}^2/\text{Vs}$.
 $n_i = 1.5 \cdot 10^{10} / \text{cm}^3$, $q = 1.602 \cdot 10^{-19} \text{ C}$,
 $\epsilon_r = 12$, $\epsilon_o = 8.85 \cdot 10^{-12} \text{ F/m}$, $V_T = 25 \text{ mV}$.




2. Study the logic circuit on the right and create the input output table. What function does this circuit realize? Why? (30 points)

3. Study DC characteristics of the 3-stage BJT amplifier circuit with $|V_{BE}| = 0,6 \text{ V}$, $h_{FE} = 200$ for all four transistors.

Do not neglect base currents. (points)

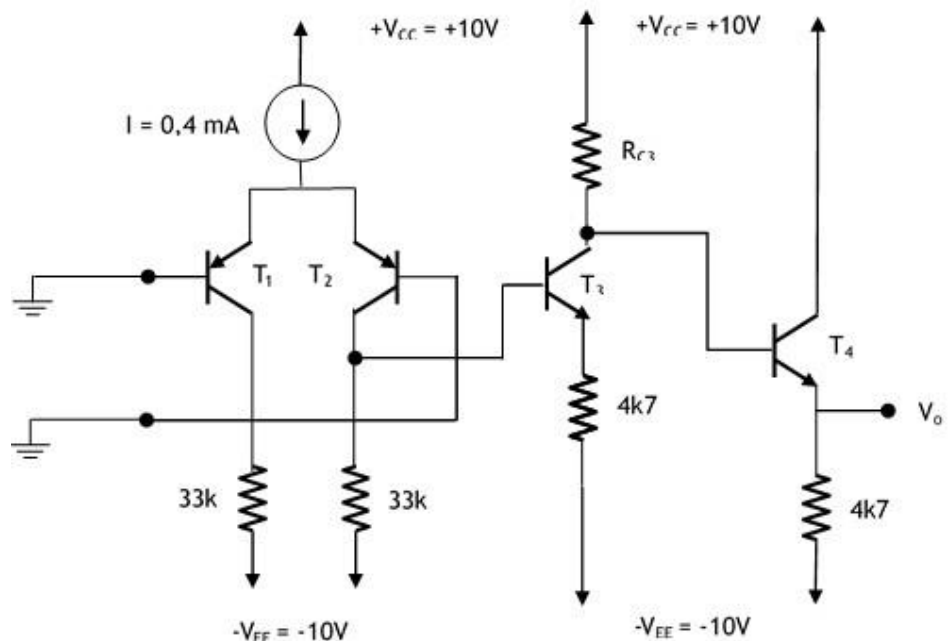- Design a current source that will provide **0,4 mA** biasing current to the differential stage. (10 points)
- Choose R_{C3} such that, T_3 is in active mode (30 points)



BONUS: Who gave these units their names and which country are they from: mH, nF, kH, C. **Each correct answer 2,5 points! Wrong answers -2,5 each!!!!**

GOOD LUCK

SOLUTIONS:

1. Using Einstein Equation, i.e., $D_{p/n} = V_T \cdot \mu_{p/n}$, we find $D_p = \underline{12 \text{ cm}^2/\text{s}}$ and $D_n = \underline{33.8 \text{ cm}^2/\text{s}}$.

$$\text{a. } V_B = V_T \cdot \ln\left(\frac{N_A \cdot N_D}{n_i^2}\right) = \underline{711 \text{ mV}}; I_o = A \cdot q \cdot n_i^2 \cdot \left[\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A}\right] = \underline{185 \text{ fA}}$$

$$\text{b. } \sigma_p = q \cdot \left(\frac{n_i^2}{N_A} \mu_n + N_A \mu_p\right) \cong q N_A \mu_p = \underline{7.69 /(\Omega \text{ cm})}$$

$$\sigma_n = q \cdot \left(N_D \mu_n + \frac{n_i^2}{N_D} \mu_p\right) \cong q N_D \mu_n = \underline{1.08 /(\Omega \text{ cm})}$$

$$\text{c. } w_{dep} = \sqrt{\frac{2 \cdot \epsilon_o \cdot \epsilon_r \cdot V_B}{q} \left(\frac{1}{N_A} + \frac{1}{N_D}\right)} = \underline{0.44 \mu\text{m}}$$

$$\text{d. with reverse at 2 V, } w_{dep} = \sqrt{\frac{2 \cdot \epsilon_o \cdot \epsilon_r \cdot (V_B + V_{bias})}{q} \left(\frac{1}{N_A} + \frac{1}{N_D}\right)} = \underline{0.87 \mu\text{m}}$$

$$\text{Thus, } C = \epsilon_o \cdot \epsilon_r \frac{A}{w} = \underline{12 \text{ pF}}$$

A	B	OUT
0	0	1
0	1	1
1	0	1
1	1	0

2. It IS A NAND GATE....

3. DC characteristics are to be studied.

a. You do your own design!

b. Without neglecting the base currents of the differential (the very first) stage, for $V_i = 0 \text{ V}$

$$I_{C1} = I_{C2} = \frac{h_{FE}}{h_{FE} + 1} \cdot \frac{I_{ref}}{2} = \frac{200}{200 + 1} \cdot \frac{0.4 \text{ mA}}{2} \Rightarrow I_{C1} = I_{C2} = \underline{0.199 \text{ mA}}$$

$$-(I_{C2} - I_{B3})33k + V_{BE3} + (h_{FE} + 1)I_{B3}4k7 = 0$$

$$I_{C3} = h_{FE} \frac{33k * I_{C2} - V_{BE3}}{(h_{FE} + 1)4k7 + 33k} = 200 \frac{33k * 0.199 \text{ mA} - 0.6 \text{ V}}{(200 + 1)4k7 + 33k} = \underline{1.2 \text{ mA}}$$

$$\text{Now we need to find the base voltage of } T_3. V_{B3} = -10 \text{ V} + (I_{C2} - I_{B3})33k = \underline{-3.63 \text{ V}}$$

For T_3 to be in active mode $V_{B3} \leq V_{C3}$. I take $V_{C3} = -3.5 \text{ V} > -3.63 \text{ V}$. Thus

$$V_{C3} = V_{B4} = -10V + 4k7 \cdot I_{E4} + V_{BE4} = -10V + 4k7 \cdot I_{B4}(h_{FE} + 1) + 0,6V = -3,5V$$

$$\Rightarrow I_{C4} = h_{FE} \cdot I_{B4} = h_{FE} \frac{10V - 3,5V - 0,6V}{4k7 \cdot (h_{FE} + 1)} = \underline{\underline{1,2mA}}$$

For T₃ to be in active mode

$$V_{C3} = -3,5V = 10V - R_{C3}(I_{C3} + I_{B4}) \Rightarrow R_{C3} \leq \frac{10V - 3,5V}{(I_{C3} + I_{B4})} = \underline{\underline{5k35}}$$