

IMPORTANT: Besides your **calculator** and the sheets you use for calculations you are only allowed to have an A4 sized “**copy sheet**” during this exam. Notes, problems and alike are not permitted. **Please submit your “copy sheet” along with your solutions.** You may get your “copy sheet” back after your solutions have been graded. **Do not forget to write down units and convert units carefully! Cell phones are not allowed and should be placed on the front desk before the exam.**

EHB222E INTRODUCTION TO ELECTRONICS (11394)


Final Exam  9 January 2016  9.00-11.00

İnci ÇİLESİZ, PhD, Hacer ATAR YILDIZ, PhD


EEF 5101, 5304

- Analyze the transistor circuit given below. BJT parameters are $V_{BE} = 0,6V$, $h_{FE} = \beta_F = 300$, $r_o = 1/h_{OE} = 34\text{ k}$ and $V_T = 25\text{ mV}$. Resistor values are $R_g = 1k$, $R_1 = 100\text{ k}$, $R_2 = 20\text{ k}$, $R_C = 2,2\text{ k}$, $R_E = 500\text{ }\Omega$, $R_Y = 10\text{ k}$ and $V_{CC} = 10\text{ V}$. Remember that C_∞ and C_E are short circuit at AC.

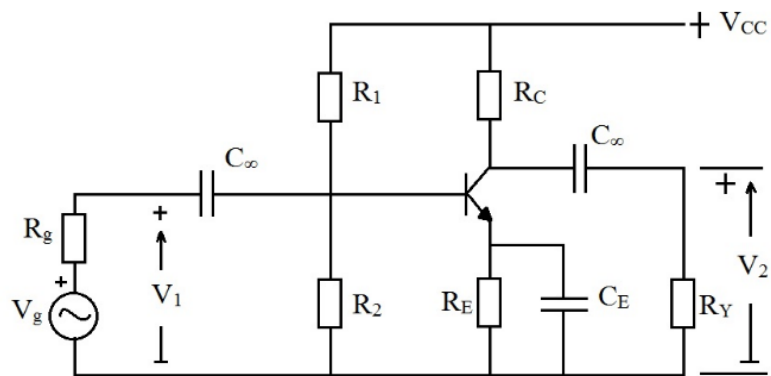- Calculate V_B , V_C , V_E and I_C .
- Find v_2/v_1 and v_2/v_g .
- Calculate **(b)** without C_E present.



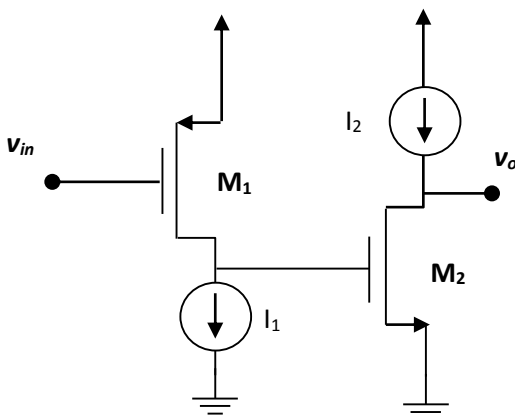
- Assuming MOS transistors below are biased by **ideal current sources**, and **both MOS are in saturation**,



- Design the two ideal current sources (using BJT or MOS to your liking)
- Calculate voltage gain v_o/v_{in} as a function of MOS parameters V_A and g_m .
- How does the gain in **(b)** change when this MOS amplifier is fed by a signal generator having a source resistance R_s , and a load R_l is connected to the output.

- Assuming the OPAMP on the right is ideal calculate V_D , V_n and V_o for $(I_{zmin} = 0\text{ mA})$

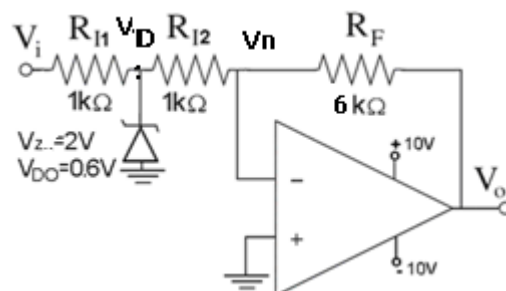- $V_i = -3\text{ V}$
- $V_i = 3\text{ V}$
- $V_i = 5\text{ V}$



GOOD LUCK

SOLUTIONS:

①

$V_{BE} = 0.6V$ $\beta = 300$
 $r_o = 34k\Omega$ $V_T = 25mV$
 $R_g = 1k\Omega$; $R_1 = 100k\Omega$; $R_2 = 20k\Omega$
 $R_C = 2k\Omega$; $R_E = 500\Omega$; $R_g = 10k\Omega$
 $V_{CC} = 10V$

a) V_C , V_B , V_E ve I_{CQ} nedir.

Çözüm:

$$R_{Th} = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2} = 16.6k\Omega$$

$$V_{Th} = \frac{V_{CC} R_2}{R_1 + R_2} = \frac{10 \cdot 20k}{120k} = 1.66V$$

$$V_{Th} = R_{Th} I_B + 0.6 + (1 + \beta) I_B R_E$$

$$1.66 = 16.6k I_B + 0.6 + 301 \cdot 500 I_B$$

$$1.06 = (16.6 + 150.5) \cdot 10^3 I_B$$

$$I_B = \frac{1.06}{167.1k} = 6.34\mu A$$

$$I_C = \beta I_B = 1.90mA$$

$$V_B = V_{BE} + (1 + \beta) R_E I_B = 0.6 + 301 \cdot 500 \cdot 6.34\mu A = 1.554V$$

$$V_E = (1 + \beta) R_E I_B = 0.954V$$

$$V_C = V_{CC} - R_C I_C = 10 - 2k \cdot 1.9mA = 5.81V$$

b) Küçük işaret aslıları:

$$R_{sig} = R_g // R_{Th}$$

$$V_2 = -g_m V_{be} \cdot R_{eq}$$

$$R_{eq} = r_o // R_C // R_E = 1.72k\Omega$$

$$V_2 = -76 \cdot 1.72k V_{be}$$

$$\frac{V_2}{V_{be}} = -130.14$$

$$V_{be} = V_1 \Rightarrow \frac{V_2}{V_1} = -130.14$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1.9mA}{25mV} = 76mS$$

$$r_c = \frac{\beta F}{g_m} = \frac{300}{76mS} = 3.94k\Omega$$


$$R_{g12} = R_{Th} // r_i = \frac{3,94k \cdot 16,6k}{(3,94 + 16,6)k} = 3,184k\Omega$$

$$V_1 = \frac{V_g \cdot R_{g12}}{R_g + R_{g12}} = \frac{V_g \cdot 3,184k}{1k + 3,184k} = 0,76 V_g$$

$$\frac{V_1}{V_g} = 0,76 \Rightarrow$$

$$\frac{V_2}{V_g} = \frac{V_2}{V_1} \cdot \frac{V_1}{V_g} = -130,14 \cdot 0,76 = -99,93$$

c) RE varken ucinaki isaret esdegeri

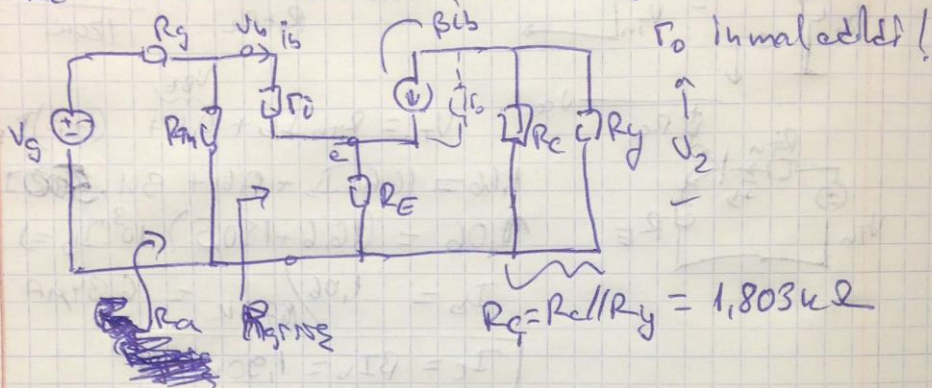

$$R_{g12} = \frac{V_b}{I_b} = r_i + (1+\beta)R_E = 154,4k\Omega$$

$$R_a = R_{g12} // R_{bh} = 154,4k\Omega // 16,6k\Omega \approx 15k\Omega$$

$$V_2 = -\beta I_b \cdot R_C = -300 \cdot 1,803k \cdot I_b = -540k \cdot I_b$$

$$V_b = V_{be} + V_e = r_i I_b + R_E (1+\beta) I_b = r_i I_b + R_E (1+\beta) I_b$$


$$V_b = (3,94k + 301 \cdot 500) I_b = 154,4k \cdot I_b$$

$$\frac{V_2}{V_b} = \frac{-540k}{154,4k} = -3,49$$

$$V_b = \frac{V_g \cdot R_a}{R_g + R_a} = \frac{V_g \cdot 15k}{(1+15)k} = 0,93 V_g \Rightarrow$$

$$\frac{V_2}{V_g} = \frac{V_2}{V_b} \cdot \frac{V_b}{V_g} = -3,49 \cdot 0,93 = -3,24$$

2. Small signal circuit:

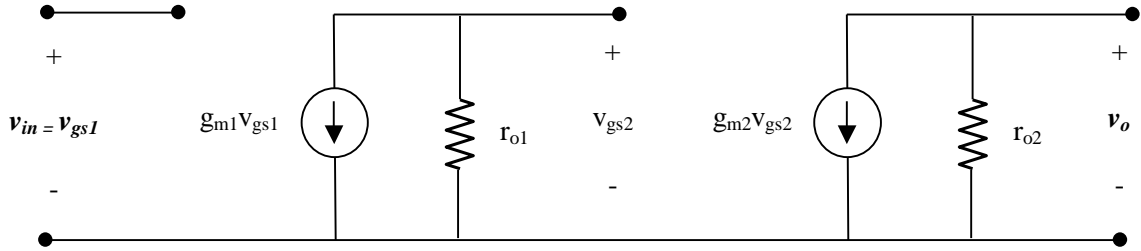

$$r_{o1} = \frac{V_{A1}}{I_{D1}}; r_{o2} = \frac{V_{A2}}{I_{D2}}$$

$$A_v = \frac{v_o}{v_{in}} = \frac{v_o}{v_{gs2}} \cdot \frac{v_{gs2}}{v_{in}} = (-g_{m2}r_{o2}) \cdot (-g_{m1}r_{o1}) = \underline{\underline{g_{m1}g_{m2}r_{o1}r_{o2}}}$$

The gain in **(b)** **does NOT** change when this MOS amplifier is fed by a signal generator having a source resistance R_s , because no current flows into the G(ate).

However, when a load R_l is connected to the output, R_l is connected in parallel to r_{o2} . Thus

$$A_v^* = \frac{v_o^*}{v_{in}} = \frac{v_o^*}{v_{gs2}} \cdot \frac{v_{gs2}}{v_{in}} = [-g_{m2}(r_{o2} \parallel R_l)] \cdot (-g_{m1}r_{o1}) = \underline{\underline{g_{m1}g_{m2}r_{o1}(r_{o2} \parallel R_l)}}$$

3. Analyze how the Zener diode works:

- The Zener diode is **forward biased**. $V_D = -V_{D0} = -0,6$ V. Assuming $V_n = 0$ V (negative feedback over the OPAMP) $V_o = -R_F/R_{I2} \cdot V_D = 3,6$ V
Because -10 V $< V_o < 10$ V **$V_n = 0$ V assumption IS CORRECT.**
- The Zener diode is reverse biased. Assuming $I_D = 0$ mA and $V_n = 0$ V, $V_D = 1,5$ V.
Since $V_D < V_Z$ **$I_D = 0$ mA assumption IS CORRECT.**
 $V_o = -R_F/R_{I2} \cdot V_D = -9$ V.
Because -10 V $< V_o < 10$ V **$V_n = 0$ V assumption IS CORRECT.**
- The Zener diode is reverse biased. Assuming $I_D = 0$ mA and $V_n = 0$ V, $V_D = 2,5$ V.
Since $V_D > V_Z$, **$I_D = 0$ mA assumption IS NOT CORRECT.**
If $I_{zmin} = 0$ mA then $V_D = V_Z = 2$ V. Assuming $V_n = 0$ V (negative feedback over the OPAMP) $V_o = -R_F/R_{I2} \cdot V_D = -12$ V. However, because -10 V $< V_o < 10$ V, $V_o = -10$ V.
THUS $V_n = 0$ V assumption IS NOT CORRECT. And $V_n = 0,28$ V