

IMPORTANT: Besides your **calculator** and the sheets you use for calculations you are only allowed to have an A4 sized **"copy sheet"** during this exam. Notes, problems and alike are not permitted. **Please submit your "copy sheet" along with your solutions.** You may get your "copy sheet" back after your solutions have been graded. **Do not forget to write down units and convert units carefully! Cell phones are not allowed and should be placed on the front desk before the exam.**


ELE222E INTRODUCTION TO ELECTRONICS (21454)

Midterm Exam #2 ✍ 5 May 2014 ⌚ 9.30-11.30


İnci ÇİLESİZ, PhD, Hacer ATAR YILDIZ, MSE

EEF 2104 and 5201

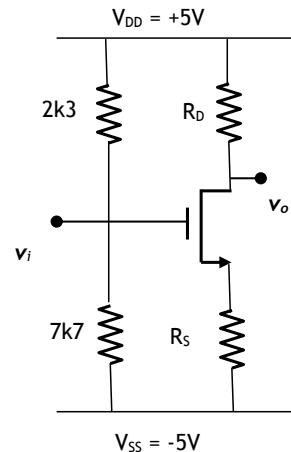1. You remember the MOS transistor shown on the circuit to the left from your first exam. The NMOS properties are $V_T = 2\text{ V}$, $V_A = \infty$, $\mu_n C_{ox} \left(\frac{W}{L}\right) = 2\text{ mA/V}^2$
 - a. Find the missing resistor values for the NMOS to operate in saturation with $I_D = 1\text{ mA}$. (10 points).
 - b. Calculate **input** and **output resistances**, gain v_o/v_i and v_o/v_s when the circuit is fed capacitively (i.e., using a capacitor to ensure that biasing conditions are not affected) with a source having an internal resistance of **1 k**. (30 points).
 - c. How can you increase the gain without changing biasing conditions? Calculate the increased gain v_o/v_i and v_o/v_s (10 points).



2. You also know the 3-stage BJT amplifier circuit from your first exam. $|V_{BE}| = 0,6\text{ V}$, $h_{FE} = h_{fe} = 200$, $h_{re} = 0$, $h_{oe} = 0$, for all four transistors. **Do NOT neglect base currents.**
 - a. Determine the value of the emitter resistor that will provide **0,4 mA biasing current** to the differential stage. (5 points)
 - b. Choose R_{C3} such that, waveform distortion at the output V_o is minimum and symmetrical, i.e., $V_o = 0\text{ V}$? (10 points)
 - c. Find the **input** and **output resistances**, the gain v_o/v_i and **CMRR**. $V_T = 25\text{ mV}$. (35 points)

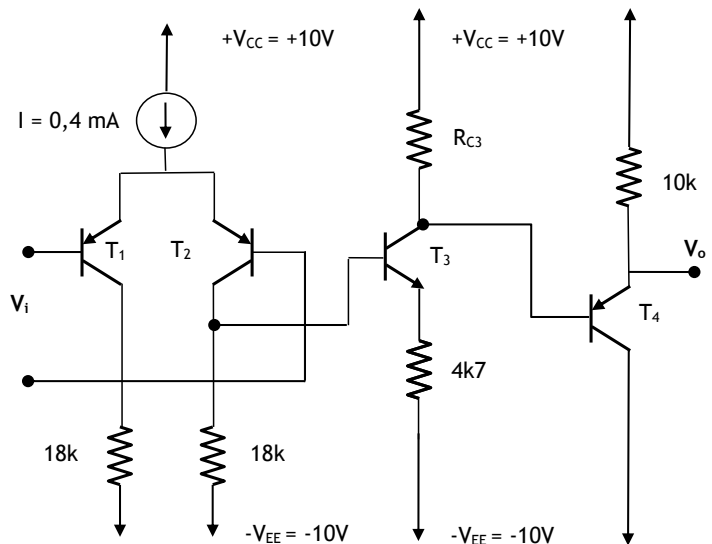

GOOD LUCK

SOLUTIONS:

1. The MOS design looks very simple BUT as you know from your first exam, many make mistakes. 2k3 and 7k7 resistors divide the 10 V voltage difference, such that $V_G = -5V + 7,7V = 2,7V$.

From the given properties it is obvious that $V_{GS} - V_t = 1V$.

Since we are working with NMOS $V_{GS} = 3V \Rightarrow V_S = V_G - V_{GS} = -0,3V \Rightarrow$

$$R_S = \frac{V_S - V_{SS}}{I_D} = \frac{-0,3V - (-5V)}{1mA} = \underline{\underline{4k7}}$$

For the NMOS to operate in saturation $V_{DS} = V_{GS} - V_t = 1V \Rightarrow V_D = V_S + 1V = -0,3 + 1 = 0,7V$

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{5V - 0,7V}{1mA} = \underline{\underline{4k3}}$$

$$Gain = \frac{v_o}{v_i} = \frac{-R_D}{1/g_m + R_S} \text{ with } g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{tn}) = 2(3 - 2) = \underline{\underline{2mA/V}} = \frac{1}{\underline{\underline{500\Omega}}}$$

$$\text{Thus } \frac{v_o}{v_i} = \frac{-R_D}{1/g_m + R_S} = \frac{-4k3}{500\Omega + 4k7} = \underline{\underline{-0,826}}$$

Realize $r_i = \frac{v_i}{i_i} \rightarrow \infty$ for the NMOS, thus $r_i^* = 2k3 \parallel 7k7 = \underline{\underline{1k77}}$, also $r_o = R_D = \underline{\underline{4k3}}$

$$\text{Since } \frac{v_s}{v_i} = \frac{r_i^*}{R_{in} + r_i^*} = \frac{1k77}{1k + 1k77} = 0,639, \frac{v_o}{v_s} = \frac{v_o}{v_i} \cdot \frac{v_i}{v_s} = \underline{\underline{-0,528}}$$

To increase gain R_s should be shorted at AC using a bridging capacitor resulting in

$$\frac{v_o}{v_i} = \frac{R_D}{1/g_m} = \frac{-4k3}{1/2mA/V} = \underline{\underline{-8,6}} \text{ and } \frac{v_o}{v_s} = \frac{v_o}{v_i} \cdot \frac{v_i}{v_s} = \underline{\underline{-5,5}}$$

2. DC characteristics are to be studied.

$$\text{a. } R_E = \frac{V_{CC} - V_E}{I} = \frac{10V - 0,6V}{0,4mA} = \underline{\underline{23k5}}$$

- b. Without neglecting the base currents of the differential (the very first) stage, for $V_i = 0V$

$$I_{C1} = I_{C2} = \frac{h_{FE}}{h_{FE} + 1} \cdot \frac{I_{ref}}{2} = \frac{200}{200 + 1} \cdot \frac{0,4mA}{2} \Rightarrow I_{C1} = I_{C2} = \underline{\underline{0,199mA}}$$

$$-(I_{C2} - I_{B3})18k + V_{BE3} + (h_{FE} + 1)I_{B3}4k7 = 0$$

$$I_{C3} = h_{FE} \frac{18k * I_{C2} - V_{BE3}}{(h_{FE} + 1)4k7 + 18k} = 200 \frac{18k * 0,199mA - 0,6V}{(200 + 1)4k7 + 18k} = \underline{\underline{0,62mA}}$$

That the output voltage is in the middle of the power supply range (+10 V and -10 V), $V_o = 0$ V

$$(h_{FE} + 1)I_{B3}R_{E4} + V_{EB4} - (I_{C3} - I_{B4})R_{C3} = 0, \text{ with } (h_{FE} + 1)I_{B4}10k = 10V \Rightarrow I_{E4} = \underline{\underline{1mA}}$$

$$(I_{C3} - I_{B4})R_{C3} = 10V + V_{EB4} \Rightarrow R_{C3} = \frac{10V + V_{EB4}}{I_{C3} - I_{B4}} = \underline{\underline{17k25}}$$

$$\text{Now the gain is } \frac{v_o}{v_i} = \frac{v_o}{v_{b3}} \cdot \frac{v_{b4}}{v_{b3}} \cdot \frac{v_{b3}}{v_i} = \frac{10k}{10k + r_{e4}} \cdot \frac{-R_{C3} \parallel r_{i4}}{4k7 + r_{e3}} \cdot \frac{18k \parallel r_{i3}}{2r_{e1/2}} \text{ with}$$

$$r_i = r_{i1/2} = 2h_{fe}r_{e1/2} = 2 \cdot 200 \cdot \frac{25mV}{0,199mA} = \underline{\underline{50k25;}}$$

$$r_{e1/2} = \underline{\underline{125,6\Omega}}$$

$$r_{e3} = \frac{25mV}{0,62mA} = 40,3\Omega;$$

$$r_{e4} = \frac{25mV}{1mA} = 25\Omega$$

$$r_{i3} = h_{fe}(r_{e3} + 4k7) = 948k$$

$$r_{i4} = h_{fe}(r_{e4} + 10k) = 2M$$

$$\text{Resulting in } \frac{v_o}{v_i} = \frac{10k}{10k + r_{e4}} \cdot \frac{-17k25 \parallel r_{i4}}{4k7 + r_{e3}} \cdot \frac{18k \parallel r_{i3}}{2r_{e1/2}} = 0,997 \cdot (-3,608) \cdot 70,307 \cong \underline{\underline{-253}}$$

$$CMRR = 20\log_{10} \left| \frac{2R_E + r_{e1/2}}{r_{e1/2}} \right| = 20\log_{10} \left| \frac{2 \cdot 23k5 + 125,6}{125,6} \right| = \underline{\underline{51,5dB}}$$