

IMPORTANT: Besides your **calculator** and the sheets you use for calculations you are only allowed to have an A4 sized **"copy sheet"** during this exam. Notes, problems and alike are not permitted. **Please submit your "copy sheet" along with your solutions.** You may get your "copy sheet" back after your solutions have been graded. **Do not forget to write down units and convert units carefully! Cell phones are not allowed and should be placed on the front desk before the exam.**


ELE222E INTRODUCTION TO ELECTRONICS (21454)

Midterm Exam #1 **31 March 2014** **9.30-11.30**


İnci ÇİLESİZ, PhD, Hacer ATAR YILDIZ, MSE

EEF 5201 and 2014

 1. Assume you are to create a diode using n- and p-typed doped silicon with the following doping parameters: $N_D = 3 \cdot 10^{17} / \text{cm}^3$, and $N_A = 10^{15} / \text{cm}^3$. You also know $L_n = 10 \mu\text{m}$, $L_p = 4 \mu\text{m}$, $\mu_n = 1600 \text{ cm}^2/\text{Vs}$, $\mu_p = 600 \text{ cm}^2/\text{Vs}$, $n_i = 1,5 \cdot 10^{10} 1/\text{cm}^3$, $q = 1,602 \cdot 10^{-19} \text{ C}$, $\epsilon_r = 12$, $\epsilon_0 = 8,85 \cdot 10^{-12} \text{ F/m}$, $V_T = 25 \text{ mV}$.
 - a. Find the barrier voltage and saturation current for a junction area of $0,1 \text{ mm}^2$. (6 points)
 - b. Calculate the specific conductivities of n- and p-type doped silicon. (6 points)
 - c. Determine the depletion zone width in **unbiased** state, when the junction is reverse biased at **4,7 V** and when it is forward biased at **0,47 V**. (9 points)
 - d. Calculate the junction capacitances for the cases in (c). (9 points)



 
2. Assuming constant voltage drop in forward bias with the barrier potential found in **Problem 1** (if you could not solve Problem 1 use 0,7 V) calculate V_o and the current flowing through D_1 (I_{D1}) for
 - a. $R_1 = 10\text{k}$ and $R_2 = 5\text{k}$, and (10 points)
 - b. $R_1 = 5\text{k}$ and $R_2 = 10\text{k}$ (10 points).



3. The MOS transistor shown on the circuit to the left has the following properties:
 $V_T = 2 \text{ V}$, $\mu_n C_{ox} \left(\frac{W}{L}\right) = 2 \text{ mA/V}^2$ Find the missing resistors values for the MOS to operate in saturation with $I_D = 1 \text{ mA}$. (20 points).

4. Study DC characteristics of the 3-stage BJT amplifier circuit with $|V_{BE}| = 0,6 \text{ V}$, $h_{FE} = 200$ for all four transistors. **Do not neglect base currents.**

 - a. Design a current source that will provide **0,4 mA** **biasing current** to the differential stage. (10 points)
- b. Choose R_{C3} such that, waveform distortion at the output V_o is minimum and symmetrical, i.e., $V_o = 0\text{V}$? (30 points)



GOOD LUCK

SOLUTIONS:

1. Using Einstein Equation , i.e., $D_p/n = V_T \mu_{p/n} \Rightarrow D_p = 15 \frac{cm^2}{s}$; $D_n = 40 \frac{cm^2}{s}$

a. $V_B = V_T \cdot \ln\left(\frac{N_A \cdot N_D}{n_i^2}\right) = \underline{\underline{698mV}}$ and

$$I_o = A \cdot q \cdot n_i^2 \cdot \left[\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right] = \underline{\underline{1,45pA}}$$

b. $\sigma_p = q \cdot \left(\frac{n_i^2}{N_A} \mu_n + N_A \mu_p \right) \cong q N_A \mu_p = \underline{\underline{0,096/(\Omega cm)}}$

$$\sigma_n = q \cdot \left(N_D \mu_n + \frac{n_i^2}{N_D} \mu_p \right) \cong q N_D \mu_n = \underline{\underline{76,9/(\Omega cm)}}$$


c. unbiased $w_{dep} = \sqrt{\frac{2 \cdot \epsilon_o \cdot \epsilon_r \cdot V_B}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right)} = \underline{\underline{0,963\mu m}}$

with reverse bias at 4,7 V, $w_{dep} = \sqrt{\frac{2 \cdot \epsilon_o \cdot \epsilon_r \cdot (V_B + V_{bias})}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right)} = \underline{\underline{2,68\mu m}}$

with forward bias at 0,47 V, $w_{dep} = \sqrt{\frac{2 \cdot \epsilon_o \cdot \epsilon_r \cdot (V_B - V_{bias})}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right)} = \underline{\underline{0,55\mu m}}$

d. Thus, $C = \epsilon_o \cdot \epsilon_r \cdot \frac{A}{w} = \begin{cases} \underline{\underline{11pF, unbiased}} \\ \underline{\underline{3,96pF, reverse @ 4,7V}} \\ \underline{\underline{19,28pF, forward @ 0,47V}} \end{cases}$

 2. Pure mathematics assuming the directions given below yield the following results for currents through resistors and diodes:



a	1,00E+04	5,00E+03	IR1	9,30E-04	ID2	2,00E-03	ID1	-1,07E-03
b	5,00E+03	1,00E+04	IR1	1,86E-03	ID2	1,00E-03	ID1	8,60E-04

NO WAY

INTERPRETATION:

- a. That means, when $R_1 = 10k$ and $R_2 = 5k$, D_2 is **NOT** conducting!

THUS, $I_{D1} = I_{R1} = \frac{10 - (-10) - 0,7}{15k} = 1,28mA$; $V_o = -10V + 5k * 1,28mA = -2,87V$

- b. When $R_1 = 5k$ and $R_2 = 10k$, $I_{D1} = I_{R1} - I_{D2} = 0,86mA$; $V_o = 0V$

3. The MOS design looks very simple BUT many make mistakes. $2k3$ and $7k7$ resistors divide the $10V$ voltage difference, such that $V_G = -5V + 7,7V = 2,7V$.

From the given properties it is obvious that $V_{GS} - V_t = 1V$.

Since we are working with NMOS $V_{GS} = 3V \Rightarrow V_S = V_G - V_{GS} = -0,3V \Rightarrow R_S = \frac{V_S - V_{SS}}{I_D} = \frac{4,7V}{1mA} = 4k7$

For the NMOS to operate in saturation $V_{DS} = V_{GS} - V_t = 1V \Rightarrow V_D = V_S + 1V = -0,3 + 1 = 0,7V$

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{5 - 0,7}{1mA} = 4k3$$

4. DC characteristics are to be studied.

- a. You do your own design!

- b. Without neglecting the base currents of the differential (the very first) stage, for $V_i = 0V$

$$I_{C1} = I_{C2} = \frac{h_{FE}}{h_{FE} + 1} \cdot \frac{I_{ref}}{2} = \frac{200}{200 + 1} \cdot \frac{0,4mA}{2} \Rightarrow I_{C1} = I_{C2} = \underline{\underline{0,199mA}}$$

$$-(I_{C2} - I_{B3})18k + V_{BE3} + (h_{FE} + 1)I_{B3}4k7 = 0$$

$$I_{C3} = h_{FE} \frac{18k * I_{C2} - V_{BE3}}{(h_{FE} + 1)4k7 + 18k} = 200 \frac{18k * 0,199mA - 0,6V}{(200 + 1)4k7 + 18k} = \underline{\underline{0,62mA}}$$

That the output voltage is in the middle of the power supply range ($+10V$ and $-10V$), $V_o = 0V$

$$(h_{FE} + 1)I_{B3}R_{E4} + V_{EB4} - (I_{C3} - I_{B4})R_{C3} = 0, \text{ with } (h_{FE} + 1)I_{B4}10k = 10V \Rightarrow I_{E4} = \underline{\underline{1mA}}$$

$$(I_{C3} - I_{B4})R_{C3} = 10V + V_{EB4} \Rightarrow R_{C3} = \frac{10V + V_{EB4}}{I_{C3} - I_{B4}} = \underline{\underline{17k25}}$$