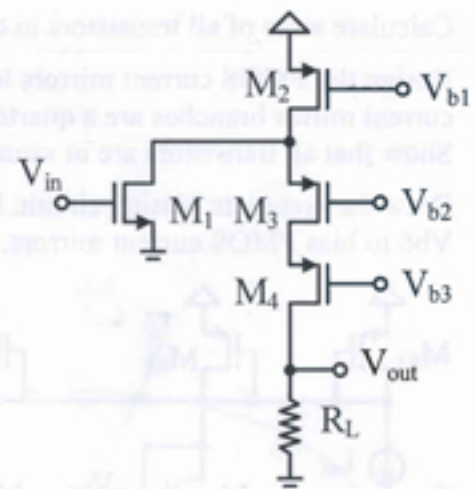


CMOS process parameters for all questions

$$V_{DD}=1.8V, C_{ox}=10\text{ fF}/\mu\text{m}^2, \mu_n=2.5\times 10^{10}\text{ }\mu\text{m}^2\text{V}^{-1}\text{s}^{-1}, \mu_p=10^{10}\text{ }\mu\text{m}^2\text{V}^{-1}\text{s}^{-1}, V_{THN}=0.4V, V_{THP}=-0.4V, \lambda_n=0.1\text{V}^{-1}, \lambda_p=0.2\text{V}^{-1}$$

1) Consider the folded cascode amplifier shown in figure 1. Please Express your answers in terms of small signal parameters of transistors.

- Determine the output resistance ( $R_{out1}$ ) of the folded cascode structure composed of M1, M2 and M3.
- Determine the equivalent transconductance ( $G_{m1}$ ) of the folded cascode structure composed of M1, M2 and M3.
- Determine the output resistance ( $R_{out}$ ) of the complete folded cascode structure composed of M1, M2, M3 and M4.
- Determine the equivalent transconductance ( $G_m$ ) of the complete folded cascode structure.
- Determine the voltage gain of the complete amplifier including  $R_L$ .



2) Consider the differential amplifier shown in figure 2.

Amplifier is perfectly symmetrical (ie. M1 and M1a are identical, M2 and M2a are identical, etc..) A common mode feedback circuit keeps current through M3, M4, M5 and M6 constant under all operating conditions and DC level of the outputs is fixed at  $V_{DD}/2$ .

Overdrive voltage ( $|V_{GS}| - |V_{TH}|$ ) is 100 mV for all transistors. Drain to source voltage is  $\pm 175$  mV for M2, M3, M6, M7, M10 and M11.  $L = 540$  nm for all transistors.

Ignore channel length modulation in all DC calculations. Use it only for small signal parameters.

$$(W/L)_9=(W/L)_{10}=200$$

$$(W/L)_1=(W/L)_5=(W/L)_6=(W/L)_7=100$$

$$(W/L)_2 = (W/L)_{11} = (W/L)_{12} = 500$$

$$(W/L)_3 = (W/L)_4 = 250$$

- a) Calculate  $V_{b1}$ ,  $V_{b2}$ ,  $V_{b3}$ ,  $V_{b4}$ ,  $V_{b5}$  and  $V_{b6}$

- c) Calculate the maximum voltage swing at the output node.

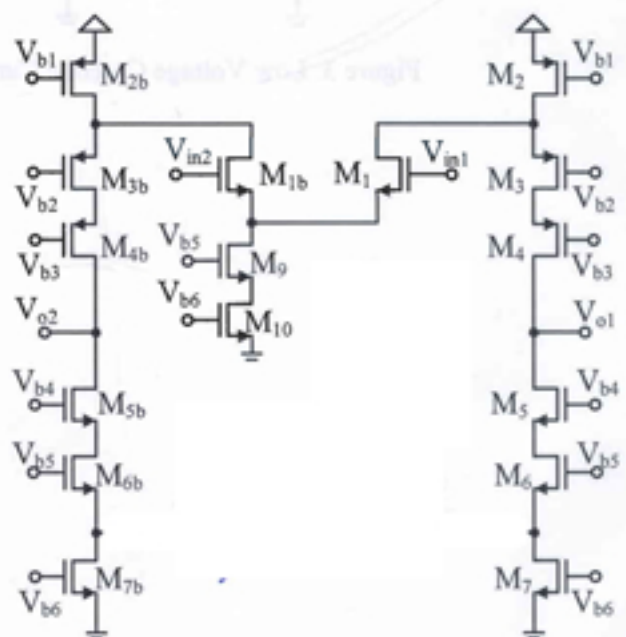


Figure 2. Folded Cascode Differential Amplifier

- d) Calculate maximum and minimum value of common mode input voltage.
  - e) Calculate  $I_D$  for each transistor.
  - f) Calculate  $g_m$  and  $r_o$  for each transistor.
  - g) Use half circuit method to split the amplifier into 2. Replace the upper and lower circuits with equivalent  $G_m$  and  $R_{out}$  values you determined in question 1.
  - h) Calculate differential voltage gain.  $(V_{o1}-V_{o2})/(V_{in1}-V_{in2})$  using half circuit method.
- 3) Current mirrors shown in figure 3 are used to generate the bias voltages  $V_{b4}$ ,  $V_{b5}$  and  $V_{b6}$ .  $M_1$ ,  $M_2$ ,  $M_3$  and  $M_{3a}$  are identical transistors.  $M_{R1}$ ,  $M_{R2}$ ,  $M_{R3}$  and  $M_{R4}$  are identical transistors.  $I_{ref}$  is half of  $I_{D7}$ .
- a)  $M_1$ ,  $M_4$  and  $M_5$  are actual diode connected transistors. In theory, same  $V_{GS}$  voltages would be generated by  $M_1$  and  $M_4$  without  $M_2$ ,  $M_3$  and  $M_{3a}$ . Explain why  $M_2$ ,  $M_3$  and  $M_{3a}$  are placed in series with the actual diode connected transistors.
  - b) Calculate sizes of all transistors in current mirrors. Show that all transistors are in saturation.
  - c) Design the PMOS current mirrors to generate  $V_{b1}$ ,  $V_{b2}$  and  $V_{b3}$ . Currents flowing in all current mirror branches are a quarter of  $I_{D2}$ . Calculate sizes of all transistors in current mirrors. Show that all transistors are in saturation.
  - d) Draw the complete biasing circuit. Use triple cascode current mirrors biased with  $V_{b4}$ ,  $V_{b5}$  and  $V_{b6}$  to bias PMOS current mirrors.

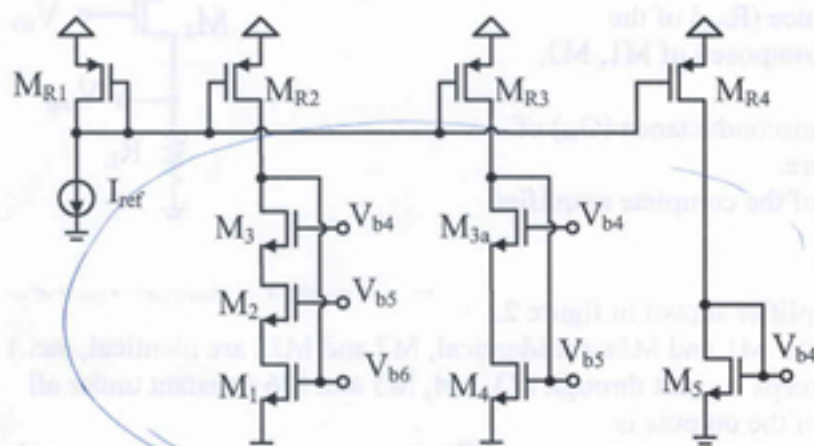


Figure 3. Low Voltage Cascode Current Mirror



$$1) a) R_{out1} = (g_{m3} r_{o3} + 1)(r_{o1} \parallel r_{o2}) + r_{o3}$$

$$b) G_{m1} = g_{m1} \cdot \frac{R_{out1} - r_{o3}}{R_{out1}}$$

$$c) A_v = G_{m1} \cdot (R_{out} \parallel R_L) = \frac{G_{m1} \cdot (R_{out} - r_{o4}) R_L}{R_{out} + R_L}$$

$$c) R_{out} = (g_{m4} r_{o4} + 1)(R_{out1}) + r_{o4}$$

$$d) G_m = G_{m1} \cdot \frac{R_{out} - r_{o4}}{R_{out}} = g_{m1} \cdot \frac{R_{out1} - r_{o3}}{R_{out1}} \cdot \frac{(R_{out} - r_{o4})}{R_{out} + R_L}$$

$$2) d) V_{b6} = V_{DD} + V_{TH7} = 500 \text{ mV}$$

$$V_{b5} = V_{DD} + V_{TH5} + V_{D7} = 675 \text{ mV}$$

$$V_{b4} = V_{DD} + V_{TH4} + V_{D7} + V_{D56} = 850 \text{ mV}$$

$$V_{b1} = V_{DD} - V_{D1} - |V_{TH2}| = 1.3 \text{ V}$$

$$V_{b2} = V_{DD} - V_{SD2} - V_{D1} - |V_{TH3}| = 1.125 \text{ V}$$

$$V_{b3} = V_{D1} - V_{SD2} - V_{SD3} - V_{D1} - |V_{TH4}| = 950 \text{ mV}$$

$$E) V_{qmax} = V_{b3} + |V_{TH4}| = 1350 \text{ mV}$$

$$V_{o,min} = V_{b4} - V_{TH5} = 450 \text{ mV}$$

$$V_{swing} = 900 \text{ mV}$$

$$d) V_{D1} = 1.625 \text{ V}$$

$$V_{Gmax} = V_{D1} + V_{TH1} = 2.025 \text{ V} \rightarrow V_{om,max} = 1.8 \text{ V}$$

$$V_{S1,min} = V_{D9,min} = V_{b5} - V_{TH9} = 275 \text{ mV}$$

$$V_{om,min} = V_{G1,min} = V_{S1,min} + V_{GS1} = 0.275 + 0.5 \text{ V} = 0.775 \text{ V}$$

$$e) I_{10} = \frac{1}{2} (2.5 \times 10^{10}) (10^{-14}) 200 (0.1)^2 = 2.5 \times 10^{-4} \text{ A}$$

$$I_2 = \frac{1}{2} (10^{10}) (10^{-14}) 500 (0.1)^2 = 2.5 \times 10^{-4} \text{ A}$$

$$I_1 = \frac{I_{10}}{2} = 125 \mu A$$

$$I_3 = I_2 - I_1 = 125 \mu A \rightarrow$$

$$I_4 = I_5 = I_6 = I_7 = I_3 = 125 \mu A$$

f) all Nmos except  $g_8$  &  $10$  are same size with same  $V_{DD}$ .

$M1-M5-M6-M7$

$$g_{m_i} = \frac{2I_D}{V_{DD}} = \frac{250 \times 10^{-6}}{0.1} = 2.5 \text{ mS}$$

$$r_o = \frac{1}{I_D \lambda_n} = \frac{1}{0.1(125 \times 10^{-4})} = 80 \text{ k}\Omega$$

$M9-M10$

$$g_m = \frac{2I_D}{V_{DD}} = 5 \text{ mS}$$

$$r_o = \frac{1}{I_D \lambda_n} = \frac{1}{0.1(25 \times 10^{-4})} = 40 \text{ k}\Omega$$

$M2$


$$g_m = \frac{2I_D}{V_{DD}} = 5 \text{ mS}$$

$$r_o = \frac{1}{I_D \lambda_p} = \frac{1}{0.1(25 \times 10^{-4})} = 20 \text{ k}\Omega$$

$M3-M4$

$$g_m = \frac{2I_D}{V_{DD}} = \frac{250 \times 10^{-6}}{0.1} = 2.5 \text{ mS} \quad r_o = \frac{1}{I_D \lambda_p} = 40 \text{ k}\Omega$$

g)

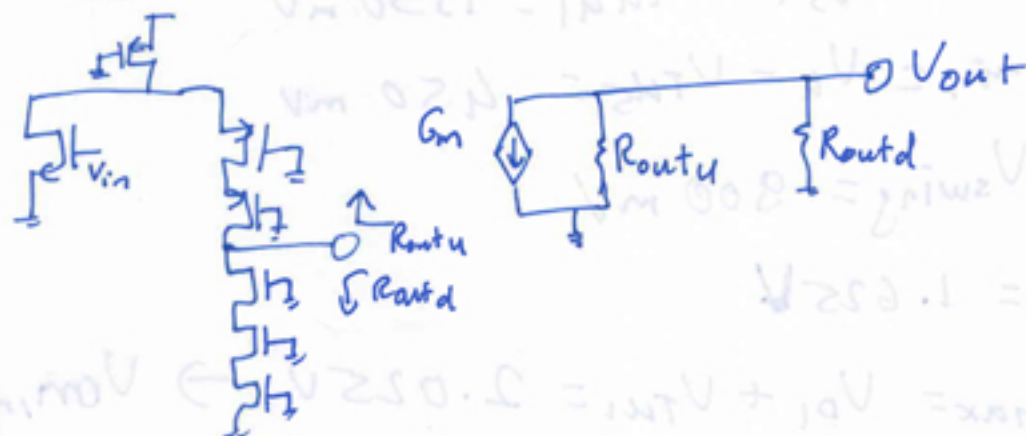

h)

From Q1

$$R_{out1} = (2.5 \text{ m}(40 \text{ k}) + 1)(80 \text{ k} \parallel 20 \text{ k}) + 40 \text{ k} = 101(16 \text{ k}) + 40 \text{ k} = 1656 \text{ k}\Omega$$

$$G_{m1} = g_{m1} \cdot \frac{R_{out1} - r_{o3}}{R_{out1}} = 2.5 \text{ m} \cdot \frac{1616 \text{ k}}{1656 \text{ k}} = 2.440 \text{ mS}$$

$$R_{outu} = (2.5 \text{ m}(40 \text{ k}) + 1)(1656 \text{ k}) + 40 \text{ k} = 167.296 \text{ M}\Omega$$

$$G_m = G_{m1} \cdot \frac{167.256}{167.296} = 2.4394 \text{ mS}$$

we said if  $r_{o1} \rightarrow \infty$ ,  $g_{m1} = G_m$ . This shows it



$$R_{outd} = (g_{m5} r_{o5} + 1) [g_{m6} r_{o6} + 1] r_{o7} + r_{o6} + r_{o5}$$

$$= 201 [201(80k) + 80k] + 80k$$

$$= (201(202) + 1) 80k = 3248.240 M\Omega$$

$$A_v = -G_m (R_{outu} || R_{outd}) = -2.4394 mS (159.1017 M\Omega)$$

$$= -388112.7 V/V$$

3) a) Channel mod. effects current mirroring performance. That is why we use cascode current mirrors.  $M_2$  &  $M_3$  makes sure  $M_1$  has exactly same drain voltage  $M_7$  or  $M_9$  has.  $M_{3a}$  makes sure  $M_4$  has exactly the same drain voltage  $M_6$  &  $M_8$  has. (in amp.)

6)  $M_1, M_2, M_3, M_{3a}$

$$I_{D1} = \frac{125 \mu A}{2} = \frac{I_{D2(amp)}}{2}$$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_3 = \frac{100}{2} \rightarrow (W/L)_7 \text{ (amp)}$$

Because they have same  $V_{GS}$ .

$$(V_{GS4c} - V_{TH}) = V_{GS} - V_{TH4} = 275 mV$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_{4c} (275 mV)^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_7 (100 mV)^2$$

$$\left(\frac{W}{L}\right)_{4c} = \frac{100}{2(275)^2} = 6.61$$

$$\left(\frac{W}{L}\right)_{sc} = 2.47$$

$$(V_{GS5c} - V_{TH}) = V_{GS} - V_{TH6} = 450 mV$$

$$(450 mV)^2 \cdot \left(\frac{W}{L}\right)_{5c} = \frac{(W/L)_7 (100 mV)^2}{2} \rightarrow \left(\frac{W}{L}\right)_{5c} = \frac{50}{(4.5)^2}$$

36)  $\rightarrow$  cont  $\Rightarrow$   $M_3$  is in SAT if

$$V_{b4} - V_{TH} < V_{b6} \Rightarrow 850 - 400 = 450 < 500$$

(If  $M_3$  is in SAT,  $M_2$  &  $M_1$  are also in SAT since their gate voltages &  $V_{th}$  are same as amplifier transistors.)

$$V_{D2} = V_{b4} - V_{GS3} = 350 \text{ mV}$$

$$V_{b5} - V_{TH} = 275 \text{ mV} < 350 \text{ mV}$$

$$V_{D1} = V_{b5} - V_{GS2} = 175 \text{ mV}$$

$$V_{b6} - V_{TH} = 100 \text{ mV} < 175 \text{ mV}$$




$$V_{D3a} = V_{b5} = 675 \text{ mV}$$

$$V_{b4} - V_{TH} = 450 \text{ mV} < 675 \text{ mV}$$

$$V_{D4} = V_{b4} - V_{GS3a} = 350 \text{ mV}$$

$$V_{b5} - V_{TH} = 275 \text{ mV} < 350 \text{ mV}$$

3) c)

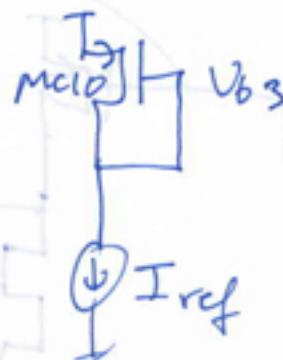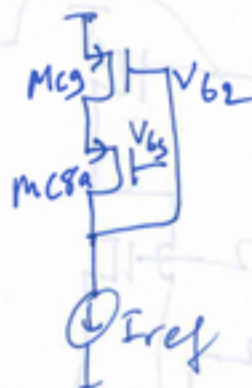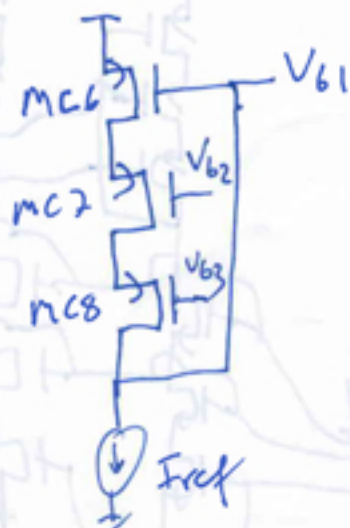

$$\left(\frac{W}{L}\right)_{C6} = \left(\frac{W}{L}\right)_{C2} = \left(\frac{W}{L}\right)_{C8} = \frac{1}{4}, \quad \left(\frac{W}{L}\right)_2 = 125 = \left(\frac{W}{L}\right)_{C8a}$$

↓  
amp

$$V_{DD} - V_{b2} - |V_{TH}| = 275 \text{ mV} = V_{DC9}$$

$$\left(\frac{W}{L}\right)_{C9} \cdot (275 \text{ mV})^2 = \frac{1}{4} \left(\frac{W}{L}\right)_2 (100 \text{ mV})^2$$

$$\left(\frac{W}{L}\right)_{C9} = \frac{500}{4(2.75)^2} = 16.53$$

$$V_{DC10} = V_{DD} - V_{b3} - |V_{TH}| = 450 \text{ mV}$$

$$\left(\frac{W}{L}\right)_{C10} = \frac{500}{4(4.5)^2} = 6.17$$

$$V_{DC9} = V_{b1} = 1300 \text{ mV.}$$

in SAT

$$V_{b3} + |V_{TH}| = 950 + 400 = 1350 \text{ mV} > 1300 \text{ mV} \quad \checkmark$$

$$V_{DC8a} = V_{b2} = 1125 \text{ mV}$$

$$V_{b3} + |V_{TH}| = 1350 \text{ mV} > 1125 \text{ mV} \quad \checkmark$$

others are all in SAT.



