

IMPORTANT: Besides your **calculator** and the sheets you use for calculations you are only allowed to have an A4 sized “**copy sheet**” during this exam. Notes, problems and alike are not permitted. **Please submit your “copy sheet” along with your solutions.** You may get your “copy sheet” back after your solutions have been graded. **Do not forget to write down units and convert units carefully! Cell phones are not allowed and should be placed on the front desk before the exam.**

EHB222E INTRODUCTION TO ELECTRONICS (20936)

Midterm Exam #1  18 March 2019  9:30-11:30

İnci ÇİLESİZ, PhD, Sadık İLİK


EEF 5105

1. Assume you are to create a diode using n- and p-typed doped silicon with the following doping parameters:
 $N_D = 3 \cdot 10^{17} / \text{cm}^3$, and $N_A = 10^{15} / \text{cm}^3$.

- Find the barrier voltage and saturation current for a junction area of $0,1 \text{ mm}^2$. (6 points)
- Calculate the specific conductivities of n- and p-type doped silicon. (6 points)
- Determine the depletion zone width in unbiased state, when the junction is reverse biased at 3,5 V and when it is forward biased at 0,35 V. (9 points)
- Calculate the junction capacitances for the cases in (c). (9 points)


$L_n = 10 \text{ } \mu\text{m}$, $L_p = 5 \text{ } \mu\text{m}$, $\mu_n = 1400 \text{ cm}^2/\text{Vs}$, $\mu_p = 500 \text{ cm}^2/\text{Vs}$, $n_i = 1.5 \cdot 10^{10} / \text{cm}^3$, $q = 1.602 \cdot 10^{-19} \text{ C}$, $\epsilon_r = 12$,
 $\epsilon_0 = 8.85 \cdot 10^{-12} \text{ F/m}$, $V_T = 25 \text{ mV}$.

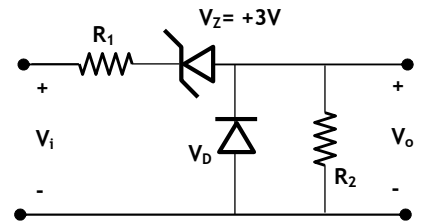2. Consider the circuit on the left. Study and plot the output voltage V_o as a function of the input voltage V_i over the range -10V to +10V. You may assume the diodes are ideal, i.e., $V_D = 0 \text{ V}$ when they are forward biased. (30 points)



3. Study DC characteristics of the 3-stage BJT amplifier circuit with $|V_{BE}| = 0,6 \text{ V}$, $h_{FE} = 200$ for all four transistors. **Do not neglect base currents.**

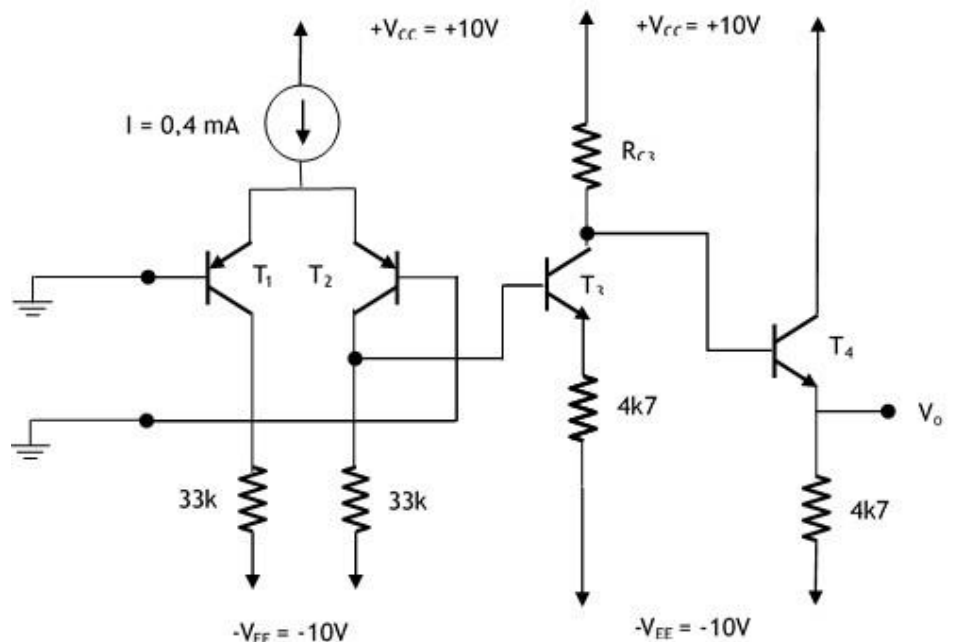- Design a current source that will provide **0,4 mA biasing current** to the differential stage. (10 points)
- Choose R_{C3} such that, T_3 is in active mode (30 points)



GOOD LUCK

SOLUTIONS:

1. Using Einstein Equation , i.e., $D_{p/n} = V_T \cdot \mu_{p/n}$, we find $D_p = \underline{12,5 \text{ cm}^2/\text{s}}$ and $D_n = \underline{35 \text{ cm}^2/\text{s}}$.

$$\text{a. } V_B = V_T \cdot \ln\left(\frac{N_A \cdot N_D}{n_i^2}\right) = \underline{698 \text{ mV}}; I_o = A \cdot q \cdot n_i^2 \cdot \left[\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A}\right] = \underline{1,26 \text{ pA}}$$

$$\text{b. } \sigma_p = q \cdot \left(\frac{n_i^2}{N_A} \mu_n + N_A \mu_p\right) \cong q N_A \mu_p = \underline{0,08 /(\Omega \text{ cm})}$$

$$\sigma_n = q \cdot \left(N_D \mu_n + \frac{n_i^2}{N_D} \mu_p\right) \cong q N_D \mu_n = \underline{67,3 /(\Omega \text{ cm})}$$

$$\text{c. unbiased } w_{dep} = \sqrt{\frac{2 \cdot \epsilon_o \cdot \epsilon_r \cdot V_B}{q} \left(\frac{1}{N_A} + \frac{1}{N_D}\right)} = \underline{0,96 \mu\text{m}}$$

$$\text{with reverse bias at 3,5 V, } w_{dep} = \sqrt{\frac{2 \cdot \epsilon_o \cdot \epsilon_r \cdot (V_B + V_{bias})}{q} \left(\frac{1}{N_A} + \frac{1}{N_D}\right)} = \underline{2,36 \mu\text{m}}$$

$$\text{with forward bias at 0,35 V, } w_{dep} = \sqrt{\frac{2 \cdot \epsilon_o \cdot \epsilon_r \cdot (V_B - V_{bias})}{q} \left(\frac{1}{N_A} + \frac{1}{N_D}\right)} = \underline{0,68 \mu\text{m}}$$

$$\text{Thus, } C = \epsilon_o \cdot \epsilon_r \cdot \frac{A}{w} = \begin{cases} \underline{11,02 \text{ pF, unbiased}} \\ \underline{4,49 \text{ pF, reverse @ 3,5V}} \\ \underline{15,61 \text{ pF, forward @ 0,35V}} \end{cases}$$

2. This circuit has to be analyzed in three parts. The plot is placed at the bottom.

- a. **-10 V < V_{in} < 0 V**: Both the regular diode and the Zener diode are forward biased. If we assume they are ideal, they effectively create electrical shorts. That is,

- i. R₁ is directly connected to R₂
- ii. both ends of R₂ are shorted
- iii. V_o = 0 V

- b. **+3 V < V_{in} < +10 V**: Both the regular diode and the Zener diode are reverse biased.


- i. the Zener diode is in the Zener zone and 3 V drops across it.
- ii. the regular diode is in cut off.

$$\text{iii. current flows over R}_1, \text{ the Zener diode and R}_2, \text{ and is } I = \frac{V_i - V_Z}{R_1 + R_2}$$

- iv. V_o = R₂I . If this current changes linearly, then V_o changes linearly.

- c. $0\text{ V} < V_{in} < +3\text{ V}$: Both the regular diode and the Zener diode are reverse biased, yet, the Zener diode is not in Zener zone.

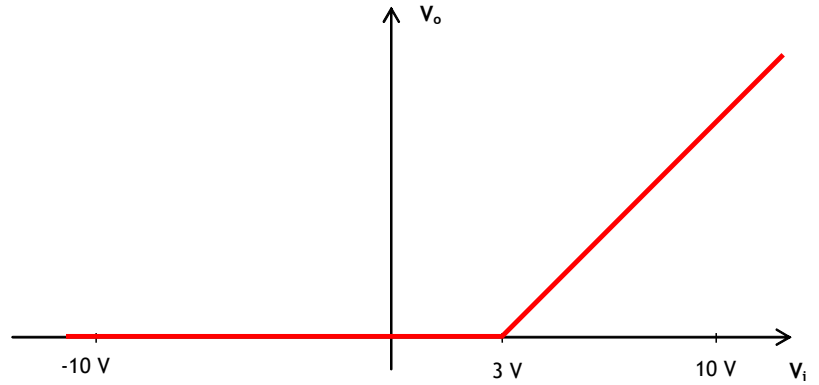- i. no current flows over R_1 , the Zener diode, the regular diode and R_2 .
- ii. $V_o = 0\text{ V}$.



3. DC characteristics are to be studied.

- a. You do your own design!
- b. Without neglecting the base currents of the differential (the very first) stage, for $V_i = 0\text{ V}$

$$I_{C1} = I_{C2} = \frac{h_{FE}}{h_{FE} + 1} \cdot \frac{I_{ref}}{2} = \frac{200}{200 + 1} \cdot \frac{0,4mA}{2} \Rightarrow I_{C1} = I_{C2} = \underline{\underline{0,199mA}}$$

$$-(I_{C2} - I_{B3})33k + V_{BE3} + (h_{FE} + 1)I_{B3}4k7 = 0$$

$$I_{C3} = h_{FE} \frac{33k * I_{C2} - V_{BE3}}{(h_{FE} + 1)4k7 + 33k} = 200 \frac{33k * 0,199mA - 0,6V}{(200 + 1)4k7 + 33k} = \underline{\underline{1,2mA}}$$

$$\text{Now we need to find the base voltage of } T_3. V_{B3} = -10V + (I_{C2} - I_{B3})33k = \underline{\underline{-3,63V}}$$

For T_3 to be in active mode $V_{B3} \leq V_{C3}$. I take $V_{C3} = -3,5V > -3,63V$. Thus

$$V_{C3} = V_{B4} = -10V + 4k7 \cdot I_{E4} + V_{BE4} = -10V + 4k7 \cdot I_{B4}(h_{FE} + 1) + 0,6V = -3,5V$$

$$\Rightarrow I_{C4} = h_{FE} \cdot I_{B4} = h_{FE} \frac{10V - 3,5V - 0,6V}{4k7 \cdot (h_{FE} + 1)} = \underline{\underline{1,2mA}}$$

For T_3 to be in active mode

$$V_{C3} = -3,5V = 10V - R_{C3}(I_{C3} + I_{B4}) \Rightarrow R_{C3} \leq \frac{10V - 3,5V}{(I_{C3} + I_{B4})} = \underline{\underline{5k35}}$$