
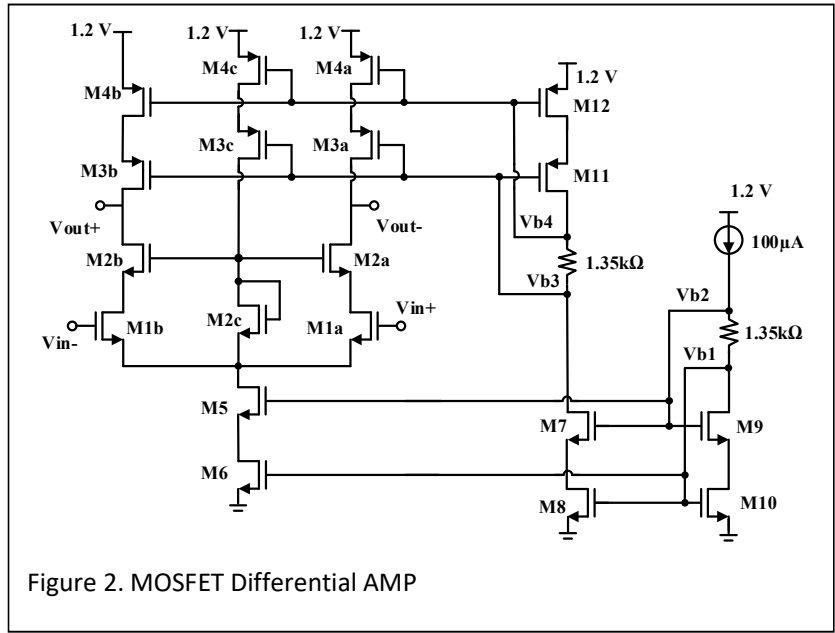


Name:

EHB 262E – MIDTERM 2

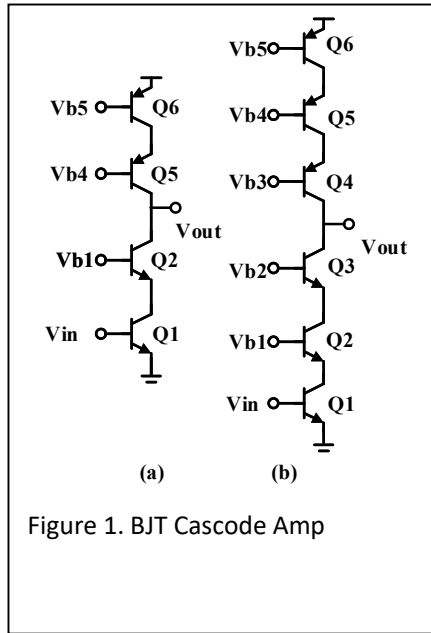

- 1) Collector current of input transistor is 1mA in each of the amplifiers in figure 1. Early voltage is 50V and β is 100 for NPNs. Early voltage is 25V and β is 50 for PNP transistors. V_T is 25mV.
 - a) Calculate I_c , g_m , r_π and r_o values for all transistors.
 - b) Calculate G_m of the input cascode, resistance of input and load cascodes.
 - c) Briefly explain why adding Q3 and Q4 does not increase the gain in BJT amplifiers.

- 2) $\mu_n = 500 \text{ cm}^2\text{V}^{-1}\text{s}^{-1}$, $\mu_p = 200 \text{ cm}^2\text{V}^{-1}\text{s}^{-1}$, $C_{ox} = 12.5 \text{ fF}/\mu\text{m}^2$, $V_{thn} = 0.3\text{V}$, $V_{thp} = -0.3\text{V}$, $\lambda_n = 0.25 \text{ V}^{-1}$, $\lambda_p = 0.5 \text{ V}^{-1}$
Overdrive voltage ($|V_{GS}| - |V_{TH}|$) is 100mV for all transistors except for M2c.

$$V_{DS1a} = V_{GS1a} - V_{TH1a} + 35\text{mV} \text{ and } V_{DS1b} = V_{GS1b} - V_{TH1b} + 35\text{mV}$$


$$W_{1a} = W_{1b} = W_{2a} = W_{2b}; \quad W_{11} = W_{12} = W_{3a} = W_{3b} = W_{4a} = W_{4b} = 2W_{3c} = 2W_{4c}; \quad W_7 = W_8 = W_9 = W_{10}$$

- a. $L = 0.5\mu\text{m}$ for all transistors. Calculate W for all transistors, currents through all transistors and V_{b1} , V_{b2} , V_{b3} and V_{b4} .
- b. Calculate the minimum value of $V_{in,CM}$. (M5-M6 must be in saturation)
- c. Calculate the maximum value of $V_{in,CM}$ which will keep M3c in SAT. Show that all M1, M2, M3, M4 transistors on both sides will be in SAT under this condition.
- d. Calculate Max and Min voltages at output
Hint: Calculate minimum output voltage for minimum $V_{in,cm}$.
- e. Use Half circuit method to split the amplifier into 2 half circuits. Calculate G_m of the input cascode, resistances of input and load cascodes.
- f. Calculate the Voltage Gain of the circuit.


Hint: If a circuit can be represented with the equivalent circuit on the left, its output resistance and transconductance is given by:

$$R_{out} = (G_2 R_2 + 1) R_1 + R_2$$
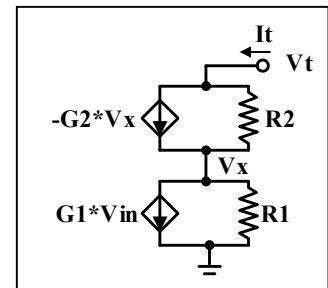
$$G_m = G_1 \frac{R_{out} - R_2}{R_{out}}$$



1)

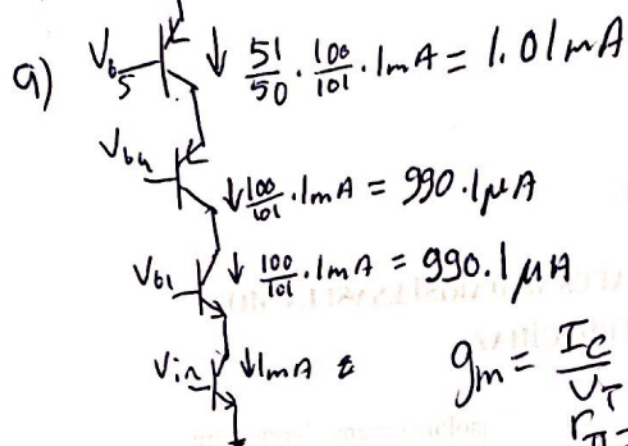


g_m	40m	39.6m	39.6m	4.04m
r_o	50k	50.5k	25.25k	24.35k
r_{π}	2500	2525	1222.5	1238

$$r_o = \frac{V_A}{I_C}$$

$$g_m = \frac{I_C}{V_T}$$

$$r_{\pi} = \beta / g_m$$

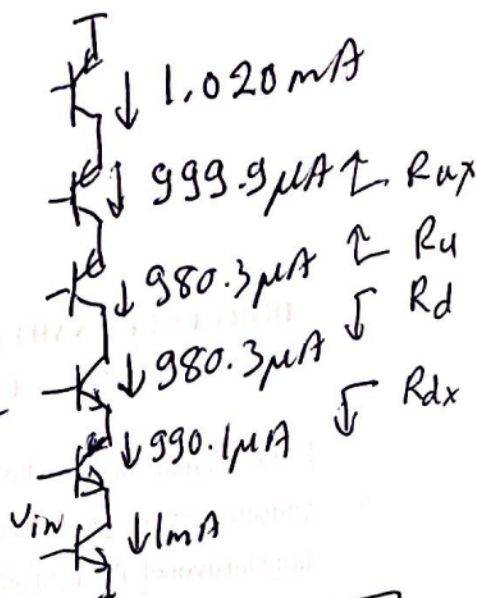

g_m	40m	39.6m	39.2m	39.2m	40m	40.8m
r_o	50k	50.5k	51k	25.5k	25k	24.5k
r_{π}	2500	2525	2550	1275	1250	1226

b) 1st

$$R_d = (g_{m2} r_{o2} + 1)(r_{o1} \parallel r_{\pi 2}) + r_{o2}$$

$$= 4.86 M\Omega$$

$$R_u = (g_{m5} r_{o5} + 1)(r_{o6} \parallel r_{\pi 5}) + r_{o5}$$

$$= 1.21 M\Omega$$

$$G_m = g_{m1} \frac{R_d - r_{o2}}{R_d} = 39.6 mS$$

2nd

$$R_{dx} = (g_{m2} r_{o2} + 1)(r_{o1} \parallel r_{\pi 2}) + r_{o2}$$

$$= 4.86 M\Omega$$

$$R_d = (g_{m3} r_{o3} + 1)(R_{dx} \parallel r_{\pi 3}) + r_{o3}$$

$$= 5.15 M\Omega$$

$$R_{ux} = (g_{m5} r_{o5} + 1)(r_{o6} \parallel r_{\pi 5}) + r_{o5}$$

$$= 1.19 M\Omega$$

$$R_u = (g_{m3} r_{o3} + 1)(R_{ux} \parallel r_{\pi 3}) + r_{o3}$$

$$= 1.275 M\Omega$$

c) Adding more than 2 transistors into cascode configuration does not increase output resistance significantly. Main reason is r_{π} resistance.

As long as emitter resistance is larger than r_{π} , their parallel combination is approximately r_{π} .

Therefore, $R_{casc} \approx (g_{m2} r_{o2} + 1)r_{\pi 2} + r_{o2}$ or $(g_{m3} r_{o3} + 1)r_{\pi 3} + r_{o3}$

$$G_{m_x} = \frac{R_{dx} - r_{o2}}{R_{dx}} \cdot g_{m1} = 39.6 mS$$

$$G_m = G_{m_x} \cdot \frac{R_d - r_{o3}}{R_d} = 39.2 mS$$

$$2) a) I_{D9} = I_{D10} = I_{D7} = I_{D8} = 100 \mu A = I_{D11} = I_{D12} = I_{D3a} = I_{D3b} = I_{D4a} = I_{D4b}$$

$$I_{D4c} = I_{D3c} = \frac{I_{D12}}{2} = 50 \mu A = I_{D2c}$$

$$I_{D5} = I_{D6} = I_{D4b} + I_{D4a} + I_{D4c} = 250 \mu A$$

$$I_{D1a} = I_{D1b} = I_{D2a} = I_{D2b} = 100 \mu A$$

$$100 \times 10^{-6} = \frac{1}{2} (500 \times 10^{-4}) (12.5 \times 10^{-3}) \left(\frac{W}{L} \right)_{10} \cdot (V_{GS10} - V_{TH})^2$$

$$V_{GS} - V_{TH} = 100 \text{ mV for all } M_x$$

$$\left(\frac{W}{L} \right)_{10} = \left(\frac{W}{L} \right)_9 = \left(\frac{W}{L} \right)_8 = \left(\frac{W}{L} \right)_7 = \left(\frac{W}{L} \right)_{1a} = \left(\frac{W}{L} \right)_{1b} = \left(\frac{W}{L} \right)_{2a} = \left(\frac{W}{L} \right)_{2b}$$

$$\left(\frac{W}{L} \right)_{10} = \frac{2 \times 10^{-4}}{62.5 \times 10^{-5} \times 10^{-2}} = 32 \quad (W_{10} = 16 \mu m)$$

$$\left(\frac{W}{L} \right)_5 = \left(\frac{W}{L} \right)_6 = \frac{2 \times (250 \times 10^{-6})}{\mu_n C_{ox} V_{DD}} = 80 \quad (W_5 = 40 \mu m)$$

$$\left(\frac{W}{L} \right)_{12} = \left(\frac{W}{L} \right)_{11} = \left(\frac{W}{L} \right)_{3a} = \left(\frac{W}{L} \right)_{3b} = \left(\frac{W}{L} \right)_{4a} = \left(\frac{W}{L} \right)_{4b} = \frac{2 \times 10^{-4}}{\mu_n C_{ox} V_{DD}} = 80$$

$$(W_{12} = 40 \mu m)$$

$$W_{4c} = W_{3c} = \frac{W_{12}}{2} = 20 \mu m$$

$$V_{b1} = V_{DD} + V_{TH} = 0.4 \text{ V}$$

$$V_{b2} = V_{b1} + 1350(10^{-4}) = 0.535 \text{ V}$$

$$V_{DD} - V_{b4} = V_{DD} + |V_{THP}| = 0.4 \text{ V}$$

$$V_{b4} = 0.8 \text{ V}$$

$$V_{b4} - V_{b3} = 1350(10^{-4}) = 0.135 \text{ V}$$

$$V_{b3} = 0.665 \text{ V}$$

$$V_{DS1a} = V_{DS1b} = 0.135V \quad V_{D1a} = V_{D1b} = V_{S1a} + 0.135V$$

$$V_{G2a} = V_{G2b} = V_{D1a} + V_{GS2a} = V_{S1a} + 0.135 + 0.4$$

$$V_{GS2c} = V_{G2a} - V_{S1a} = 0.535V = V_{S1a} + 0.535V_{ms}$$

$$\left(\frac{W}{L}\right)_{2c} = \frac{2 \times 5 \times 10^{-5}}{\mu_n C_{ox} (V_{GS2c} - V_{TH})} = 2.9 \quad (15)$$

$$W_{2c} = 1.45 \mu m$$

$$b) V_{DS_{min}} = V_{G2} - V_{TH} = 0.235V = V_{S1a_{min}} \quad (7.5)$$

$$V_{in_{cm_{min}}} = V_{DS_{min}} + V_{GS1a} = 0.635V$$

$$c) V_{D2c} = V_{G2c} = V_{S1a} + 0.535V = V_{G1a} - V_{GS1a} + 0.535V$$

$$= V_{G1a} + 0.135V \quad (7.5)$$

$$V_{D2c_{max}} = V_{D3c_{max}} = V_{G3} + |V_{THP}| = 0.965V$$

$$V_{G1a_{max}} = V_{D3c_{max}} - 0.135 = 0.830V$$


$$2d) V_{Omax} = V_{b3} + |V_{THP}| = 0.965V$$

(10)

$$V_{G2amin} = V_{G2Cmin} = V_{S1amin} + V_{GS2C} = 0.235 + 0.535 = 0.77V$$

$$V_{Omin} = V_{G2amin} - V_{TH} = 0.47V$$

e)

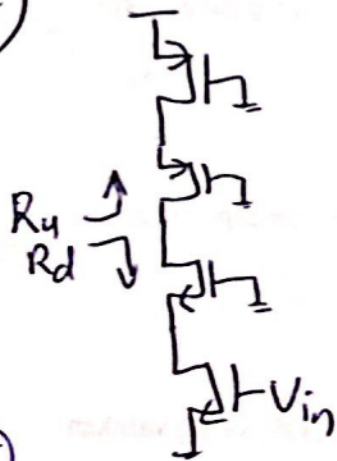

Since $I_{D4C} = I_{D2C}$ is DC, V_{GS2C} is constant. When a diff input is applied, V_{S1a} is AC ground. Thus, V_{G2a} is also AC ground.

(15)

$$R_d = (g_{m2a} r_{o2a} + 1) r_{o1a} + r_{o2a} = 81(40k) + 40k = 3.28 M\Omega$$

$$R_u = (g_{m3a} r_{o3a} + 1) r_{o4a} + r_{o3a} = 840 k\Omega$$

$$G_m = g_{m1a} \cdot \frac{R_d - r_{o2a}}{R_d} = 1.98 mS$$

$$g_m = \frac{2I_D}{V_{DD}}$$

$$g_{m1} = g_{m2} = g_{m3} = g_{m4} = 2 mS$$

$$r_o = \frac{1}{\lambda I_D}$$

$$r_{o1} = r_{o2} = \frac{1}{0.25(10^{-4})} = 40 k\Omega$$

$$r_{o3} = r_{o4} = \frac{1}{0.5(10^{-4})} = 20 k\Omega$$

$$f) A_v = -G_m(R_d || R_u) = 1320 V/V$$

(10)