

**IMPORTANT:** Besides your **calculator** and the sheets you use for calculations you are only allowed to have an A4 sized “**copy sheet**” during this exam. Notes, problems and alike are not permitted. **Please submit your “copy sheet” along with your solutions.** You may get your “copy sheet” back after your solutions have been graded. **Do not forget to write down units and convert units carefully! Cell phones are not allowed and should be placed on the front desk before the exam.**


## EHB222E INTRODUCTION TO ELECTRONICS (20727)

**Midterm Exam #1** ✎ **23 March 2015** ⌚ **9.30-11.30**


**İnci ÇİLESİZ, PhD, Can ZOROĞLU, BS**

**EEF 2014**

 1. Assume you have a diode made of n- and p-typed doped silicon with the following parameters:  $\mu_n = 1600 \text{ cm}^2/\text{Vs}$ ,  $\mu_p = 600 \text{ cm}^2/\text{Vs}$ ,  $n_i = 1,5 \cdot 10^{10} \text{ 1/cm}^3$ ,  $q = 1,602 \cdot 10^{-19} \text{ C}$ ,  $\epsilon_r = 12$ ,  $\epsilon_o = 8,85 \cdot 10^{-12} \text{ F/m}$ ,  $V_T = 25 \text{ mV}$ .
  - a. Find the dopant densities for n- and p-type silicon for specific resistances of  $1 \Omega\text{cm}$  and  $0,5 \Omega\text{cm}$  respectively. (6 points)
  - b. Find the barrier voltage and saturation current for a junction area of  $0,15 \text{ mm}^2$ . (6 points)
  - c. Determine the depletion zone width in **unbiased** state, when the junction is reverse biased at **2,5 V** and when it is forward biased at **0,25 V**. (9 points)
  - d. Calculate the junction capacitances for the cases in (c). (9 points)
2. For the circuit shown on the right sketch  $V_{out}$  as a function of  $V_{in}$  for  $V_{in}$ :  $-10 \text{ V}$  to  $+10 \text{ V}$  assuming all three resistors are  $10\text{k}$  and the voltage drop across conducting diodes are constant at  $0,6 \text{ V}$ . (30 points)  
HINT: Analyze the circuit first at  $V_{in} = 0\text{V}$ ; then at  $+10 \text{ V}$  and  $-10 \text{ V}$ , and finally at values in between.



3. Study DC characteristics of the 3-stage BJT amplifier circuit with  $|V_{BE}| = 0,6 \text{ V}$ ,  $h_{FE} = 200$  for all four transistors. **Do not neglect base currents.**
  - a. Design a current source that will provide **0,4 mA** biasing current to the differential stage. (10 points)
  - b. Choose  $R_{C3}$  such that, waveform distortion at the output  $V_o$  is minimum and symmetrical, i.e.,  $V_o = 0\text{V}$ ? (30 points)

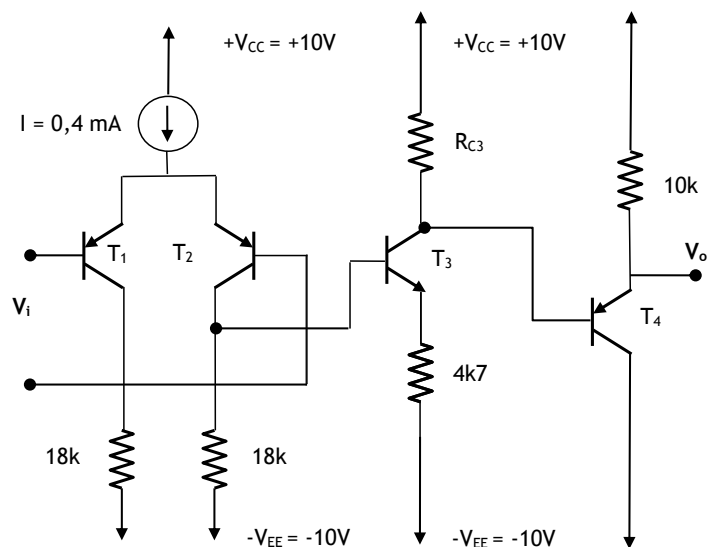

**GOOD LUCK**

**SOLUTIONS:**

1. Using Einstein Equation , i.e.,  $D_p/n = V_T \mu_{p/n} \Rightarrow D_p = 15 \frac{cm^2}{s}$ ;  $D_n = 40 \frac{cm^2}{s}$

$$a. \quad \sigma_p = q \cdot \left( \frac{n_i^2}{N_A} \mu_n + N_A \mu_p \right) \cong q N_A \mu_p \Rightarrow N_A = \frac{\sigma_p}{q \mu_p} = \underline{\underline{2,08 \cdot 10^{16} / cm^3}}$$

$$\sigma_n = q \cdot \left( N_D \mu_n + \frac{n_i^2}{N_D} \mu_p \right) \cong q N_D \mu_n \Rightarrow N_D = \frac{\sigma_n}{q \mu_n} = \underline{\underline{3,9 \cdot 10^{15} / cm^3}}$$

$$b. \quad V_B = V_T \cdot \ln \left( \frac{N_A \cdot N_D}{n_i^2} \right) = \underline{\underline{665 mV}} \text{ and } I_o = A \cdot q \cdot n_i^2 \cdot \left[ \frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right] = \underline{\underline{625 fA}}$$

$$c. \quad \text{unbiased } w_{dep} = \sqrt{\frac{2 \cdot \epsilon_o \cdot \epsilon_r \cdot V_B}{q} \left( \frac{1}{N_A} + \frac{1}{N_D} \right)} = \underline{\underline{0,51 \mu m}}$$


$$\text{with reverse bias at 2,5 V, } w_{dep} = \sqrt{\frac{2 \cdot \epsilon_o \cdot \epsilon_r \cdot (V_B + V_{bias})}{q} \left( \frac{1}{N_A} + \frac{1}{N_D} \right)} = \underline{\underline{1,13 \mu m}}$$

$$\text{with forward bias at 0,25 V, } w_{dep} = \sqrt{\frac{2 \cdot \epsilon_o \cdot \epsilon_r \cdot (V_B - V_{bias})}{q} \left( \frac{1}{N_A} + \frac{1}{N_D} \right)} = \underline{\underline{0,41 \mu m}}$$


$$d. \quad \text{Thus, } C = \epsilon_o \cdot \epsilon_r \cdot \frac{A}{w} = \begin{cases} \underline{\underline{30,74 pF, unbiased}} \\ \underline{\underline{14 pF, reverse @ 2,5V}} \\ \underline{\underline{38,9 pF, forward @ 0,25V}} \end{cases}$$

 2. Assume there is no  $V_{in}$ .  $V_{out} = 0V$  because of the symmetry of the circuit, and because all diodes are conducting. This is the same as  $V_{in} = 0V$ . Now assume  $V_{in} = 10V$ . We can easily see that  $D_1$  and  $D_3$  are reverse biased because most of the voltage drop from  $+10V$  to  $-10V$  is over the resistors  $R_1$  and  $R_2$ . In other words, the anode of  $D_1$  is much less than  $+10V$  whereas the cathode is at  $+10V$  (reverse bias). Also,  $D_4$  is conducting, thus, the cathode of  $D_3$  is at  $9,4V$  whereas the anode of  $D_3$  is much less than  $+9,4V$ . That means current flows (a) from  $+10V$  over  $R_1$ ,  $D_2$ , and  $R_3$  to ground (follow blue line), and (b) from  $V_{in}$  over  $D_4$  and  $R_4$  to  $-10V$ . Since only  $0,6V$  drops on the conducting diodes  $9,4V$  drops over the two resistors  $R_1$  and  $R_3$ . Since  $R_1$  and  $R_3$  have equal values, we divide the voltage drop by 2 and this is  $V_{out} = 4.7V$ .

Now assume  $V_{in} = -10V$ . Similar to the observations above,  $D_4$  and  $D_2$  are reverse biased because most of the voltage drop from  $+10V$  to  $-10V$  is again over the resistors  $R_1$  and  $R_2$ . In other words, the cathode of  $D_4$  is much higher than  $-10V$  whereas the anode is at  $-10V$  (reverse bias again). Also,  $D_1$  is conducting, thus, the anode of  $D_2$  is at  $-9,4V$  whereas the cathode of  $D_2$  is much higher than  $-9,4V$ . That means current flows (a) from the ground over  $R_3$ ,  $D_3$ , and  $R_2$  to  $-10V$  (follow red line), and (b) from  $+10V$  over  $R_1$  and  $D_1$  to  $V_{in}$ . Since only  $0,6V$  drops on the conducting diodes  $9,4V$  drops over the two resistors  $R_2$  and  $R_3$ . Since  $R_2$  and  $R_3$  have equal values, we divide the voltage drop by 2 and this is  $V_{out} = 4.7V$ .



 Finally, we need to consider the output for  $0V \geq V_{in} \geq -10V$  and  $0V \leq V_{in} \leq +10V$ . One sees easily that when all the 4 diodes are conducting, the output  $V_{out}$  follows the input  $V_{in}$  because the circuit is symmetrical. When do all the 4 diodes conduct? See the sketch below....Capito???



3. DC characteristics are to be studied.

- You do your own design!
- Without neglecting the base currents of the differential (the very first) stage, for  $V_i = 0V$

$$I_{C1} = I_{C2} = \frac{h_{FE}}{h_{FE} + 1} \cdot \frac{I_{ref}}{2} = \frac{200}{200 + 1} \cdot \frac{0,4mA}{2} \Rightarrow I_{C1} = I_{C2} = \underline{\underline{0,199mA}}$$

$$-(I_{C2} - I_{B3})18k + V_{BE3} + (h_{FE} + 1)I_{B3}4k7 = 0$$

$$I_{C3} = h_{FE} \frac{18k * I_{C2} - V_{BE3}}{(h_{FE} + 1)4k7 + 18k} = 200 \frac{18k * 0,199mA - 0,6V}{(200 + 1)4k7 + 18k} = \underline{\underline{0,62mA}}$$

That the output voltage is in the middle of the power supply range (+10V and -10V),  $V_o = 0V$

$$(h_{FE} + 1)I_{B3}R_{E4} + V_{EB4} - (I_{C3} - I_{B4})R_{C3} = 0, \text{ with } (h_{FE} + 1)I_{B4}10k = 10V \Rightarrow I_{E4} = \underline{\underline{1mA}}$$

$$(I_{C3} - I_{B4})R_{C3} = 10V + V_{EB4} \Rightarrow R_{C3} = \frac{10V + V_{EB4}}{I_{C3} - I_{B4}} = \underline{\underline{17k25}}$$