
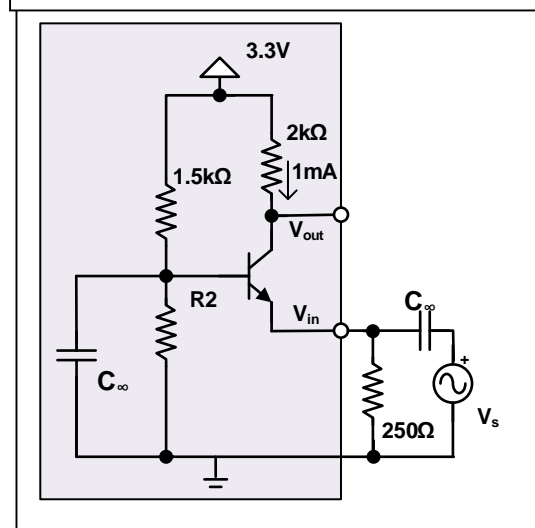


Name:


Student ID:

EHB 262E ELECTRONICS 2

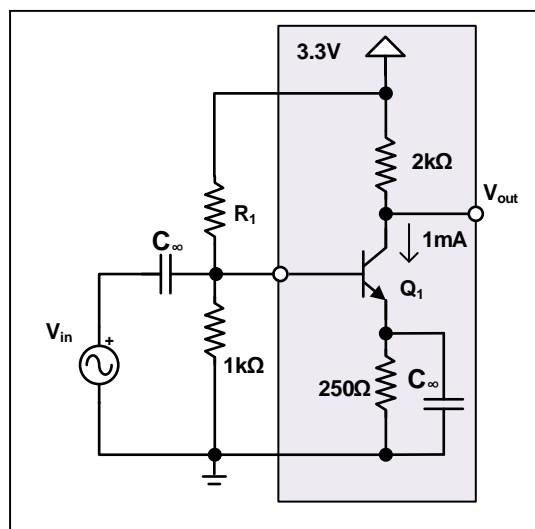1. $\beta=80$; $V_A=50V$; $I_c=1\text{ mA}$; $I_s=6.91 \times 10^{-16}\text{ A}$; $V_T=25\text{ mV}$
 - a) Calculate all DC voltages and R_1 .
 - b) Calculate G_m , R_{out} and unloaded voltage gain for the amplifier.
 - c) Assume an R_L resistor is connected to the output. Express R_{in} (excluding biasing resistors) as a function of R_L .
2. $\beta=80$; $V_A=50V$; $I_c=1\text{ mA}$; $I_s=6.91 \times 10^{-16}\text{ A}$; $V_T=25\text{ mV}$
 - a) Calculate all DC voltages and R_2 .
 - b) Calculate G_m , R_{out} and unloaded voltage gain for the amplifier.
 - c) Assume an R_L resistor is connected to the output. Express R_{in} as a function of R_L .
Hint: Treat 250Ω resistor as an external resistor connected in parallel with the amplifier input. Don't include it in the R_{in} calculation.




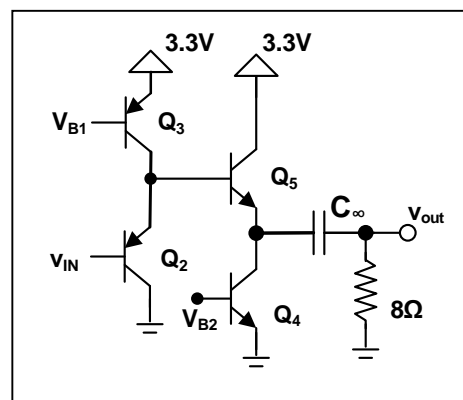3. $\beta_2=\beta_3=60$; $\beta_4=\beta_5=80$; $V_{A2}=V_{A3}=30V$; $V_{A4}=V_{A5}=50V$; $V_{B1}=2.6V$; $V_{B2}=0.7V$; $I_{s2}=I_{s3}=6.91 \times 10^{-16}\text{ A}$; $I_{s4}=I_{s5}=3.455 \times 10^{-14}\text{ A}$
 - a) Input resistance of the voltage buffer shown in figure 3 while driving a 8Ω load resistor.
 - b) Calculate the voltage gain of the buffer.
4. Assume you want to drive an 8Ω speaker with a signal source with 500Ω output resistance and a peak to peak voltage of 10mV .
 - a) You connect the amplifier in Q1 and the buffer in Q3 and drive the 8Ω resistor. Calculate the peak to peak voltage applied to the load resistor.
 - b) You connect the amplifier in Q2 and the buffer in Q3 and drive the 8Ω resistor. Calculate the peak to peak voltage applied to the load resistor. 250Ω resistor is still connected to the input of the amplifier.
 - c) Why is there such a big difference between output signals of these 2 structures?



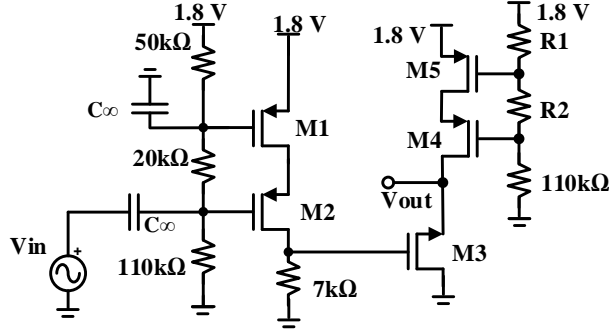5. $\mu_n = 0.05 \text{ m}^2\text{V}^{-1}\text{s}^{-1}$, $\mu_p = 0.02 \text{ m}^2\text{V}^{-1}\text{s}^{-1}$, $C_{ox} = 0.0125 \text{ F/m}^2$, $V_{thn} = 0.4\text{V}$, $V_{thp} = -0.4\text{V}$, $\lambda_n = 0.15 \text{ V}^{-1}$, $\lambda_p = 0.3 \text{ V}^{-1}$

$W_1 = W_2 = 40\mu\text{m}$; $W_3 = W_4 = W_5 = 100\mu\text{m}$; All L are $0.5\mu\text{m}$



- Determine values for R1, R2, which will keep M6 in SAT and 100mV away from edge of triode region if $I_{D4} = I_{D5}$ is 1mA.
- Calculate DC voltages of all nodes in circuit.
- Calculate DC currents in all branches.
- Calculate the Voltage Gain of the circuit.

Equations:

Common Emitter Amplifier:
$$R_{in} = r_{\pi} + \frac{(1 + \beta) R_E r_o + R_E (R_C \parallel R_L)}{R_E + (R_C \parallel R_L) + r_o}$$

$$R_{out} = (g_m r_o (R_E \parallel r_{\pi}) + R_E \parallel r_{\pi} + r_o) \parallel R_C \quad G_m = \frac{g_m r_o r_{\pi} - R_E}{(r_{\pi} + R_E)((g_m r_o + 1)(r_{\pi} \parallel R_E) + r_o)}$$

Common Base Amplifier:
$$R_{in} = r_{\pi} \parallel \left(\frac{r_o + R_C \parallel R_L}{g_m r_o + 1} \right) \quad R_{out} = r_o \parallel R_C \quad G_m = -\frac{g_m r_o + 1}{r_o}$$

Emitter Follower:
$$R_{in} = (\beta + 1)(r_o \parallel R_E \parallel R_L) + r_{\pi} \quad R_{out} = \frac{1}{g_m} \parallel r_{\pi} \parallel R_E \parallel r_o \quad G_m = -\frac{g_m r_{\pi} + 1}{r_{\pi}}$$

Common Source Amplifier:
$$R_{in} = \infty \quad R_{out} = (g_m r_o R_S + R_S + r_o) \parallel R_D$$

$$G_m = \frac{g_m r_o}{(g_m r_o + 1) R_S + r_o}$$

Common Gate Amplifier:
$$R_{in} = \frac{r_o + R_D \parallel R_L}{g_m r_o + 1} \quad R_{out} = r_o \parallel R_D \quad G_m = -\frac{g_m r_o + 1}{r_o}$$

Emitter Follower:
$$R_{in} = \infty \quad R_{out} = \frac{1}{g_m} \parallel R_S \parallel r_o \quad G_m = -g_m$$

Gain:
$$A_v = -G_m (R_{out} \parallel R_L)$$

$$I_C = I_S \exp\left(\frac{|V_{BE}|}{V_T}\right) \quad I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (|V_{GS}| - |V_{TH}|)^2$$

Soln

$$1) \ a) \ I_B = \frac{I_C}{\beta} = \frac{10^{-3}}{80} = 12.5 \mu A$$

$$V_C = V_{CC} - I_C R_C = 3.3 - 2000(10^{-3}) = 1.3V$$

$$V_E = I_E R_E = 250(1.0125 \times 10^{-3}) = 253.125mV$$

$$V_{BE} = V_T \ln \left(\frac{I_C}{I_S} + 1 \right) = 700.016mV$$

$$V_B = V_E + V_{BE} = 953.141mV$$

$$R_1 = \frac{V_{CC} - V_B}{I_B + \frac{V_B}{1k\Omega}} = 2430.36\Omega$$

b) $G_m = g_{m1}$ for common source amplifier

$$G_m = g_{m1} = \frac{I_C}{V_T} = 40mS$$

$$r_{o1} = \frac{V_A}{I_C} = 50k\Omega$$

$$R_{out} = r_o \parallel R_C = 50k\Omega \parallel 2k\Omega = 1923.08\Omega$$

$$A_v = -G_m R_{out} = -76.92V/V$$

$$c) \ R_{in} = r_{\pi} + R_E \frac{(\beta + 1)r_o + (R_C \parallel R_L)}{r_o + (R_C \parallel R_L) + R_E}$$

R_E is shorted to ground in this amplifier, so this equation simplifies to

$$R_{in} = r_{\pi1} = 2k\Omega$$

$$2) \ a) \ I_B = \frac{I_C}{\beta} = \frac{10^{-3}}{80} = 12.5 \mu A$$

$$V_C = V_{CC} - I_C R_C = 3.3 - 2000(10^{-3}) = 1.3V$$

$$V_E = I_E R_E = 250(1.0125 \times 10^{-3}) = 253.125mV$$

$$V_{BE} = V_T \ln \left(\frac{I_C}{I_S} + 1 \right) = 700.016mV$$

$$V_B = V_E + V_{BE} = 953.141mV$$

$$R_2 = \frac{V_B}{\frac{V_{CC} - V_B}{1.5k\Omega} - I_B} = 614.11\Omega$$

$$b) \ g_{m1} = \frac{I_C}{V_T} = 40mS$$

$$r_{o1} = \frac{V_A}{I_C} = 50k\Omega$$

$$G_m = -g_{m1} - \frac{1}{r_{o1}} = -40.02mS$$

$$R_{out} = r_o \parallel R_C = 50k\Omega \parallel 2k\Omega = 1923.08\Omega$$

$$A_v = -G_m R_{out} = 76.96V/V$$

$$c) R_{in} = r_\pi \parallel \frac{r_{o1} + (R_C \parallel R_L)}{g_{m1} r_{o1} + 1}$$

$$R_{in} = 2000 \parallel \frac{50k\Omega + (2000 \parallel R_L)}{2001}$$

RL in parallel with 2kΩ will be less than 2kΩ. This will be small compared to 50kΩ. Therefore, Rin will be relatively independent of RL.

3) a) First determine collector currents of all 4 transistors

$$I_{C4} = I_{s4} \left(\exp \left(\frac{V_{BE4}}{V_T} \right) - 1 \right) = 49.968mA$$

$$I_{C5} = \frac{\beta_5}{\beta_5 + 1} I_{E5} = \frac{\beta_5}{\beta_5 + 1} I_{C4} = 49.351mA$$

$$I_{B5} = \frac{I_{E5}}{\beta_5 + 1} = 617\mu A$$

$$I_{C3} = I_{s3} \left(\exp \left(\frac{|V_{BE3}|}{V_T} \right) - 1 \right) = 999.36\mu A$$

$$I_{E2} = I_{C3} - I_{B5} = 382.4\mu A$$

$$I_{C2} = \frac{\beta_2}{\beta_2 + 1} I_{E2} = 376.20\mu A$$

$$g_{m5} = \frac{I_{C5}}{V_T} = 1.9741S$$

$$r_{o5} = \frac{V_{A5}}{I_{C5}} = 1013.15\Omega$$

$$r_{\pi5} = \frac{V_T}{I_{B5}} = 40.526\Omega$$

$$g_{m4} = \frac{I_{C4}}{V_T} = 1.9987S$$

$$r_{o4} = \frac{V_{A4}}{I_{C4}} = 1000.64\Omega$$

$$r_{\pi4} = \frac{V_T}{I_{B4}} = 40.025\Omega$$

$$g_{m3} = \frac{I_{C3}}{V_T} = 39.975mS$$

$$r_{o3} = \frac{V_{A3}}{I_{C3}} = 30019.1\Omega$$

$$r_{\pi3} = \frac{V_T}{I_{B3}} = 1500.96\Omega$$

$$g_{m2} = \frac{I_{C2}}{V_T} = 1.5048mS$$

$$r_{o2} = \frac{V_{A2}}{I_{C2}} = 79744.3\Omega$$

$$r_{\pi2} = \frac{V_T}{I_{B2}} = 3987.2\Omega$$

Rin2 is resistance seen looking into base of Q5.

$$R_{in2} = r_{\pi5} + (\beta_5 + 1)(r_{o4} \parallel r_{o5} \parallel R_L) = 678.39\Omega$$

$$R_{in} = r_{\pi2} + (\beta_2 + 1)(r_{o2} \parallel r_{o3} \parallel R_{in2}) = 44120.6\Omega$$

b) We have 2 Emitter Follower stages cascaded.

$$G_{m1} = - \left(g_{m2} + \frac{1}{r_{\pi2}} \right) = -15.30mS$$

$$R_{out1} = \frac{1}{g_{m2}} \parallel r_{o2} \parallel r_{\pi2} \parallel r_{o3} = 65.17\Omega$$

$$G_{m2} = -\left(g_{m5} + \frac{1}{r_{\pi5}}\right) = -1.9987S$$

$$R_{out2} = \frac{1}{g_{m5}} \parallel r_{o5} \parallel r_{\pi5} \parallel r_{o4} = 0.4998\Omega$$

$$A_{v1} = -G_{m1} (R_{out1} \parallel R_{in2}) = 0.90963V/V$$

$$A_{v2} = -G_{m2} (R_{out2} \parallel R_L) = 0.94026V/V$$

$$A_v = A_{v1} A_{v2} = 0.8553V/V$$

4) a) $R_{in,Q1B} = r_{\pi1} = 2k\Omega$ Resistance seen looking into base of Q1 in Question 1

$$R_{in,CE} = R_{in,Q1B} \parallel R_1 \parallel R_2 = 2k\Omega \parallel 2.43k\Omega \parallel 1k\Omega = 523.16\Omega$$

Input voltage of the CE amplifier is determined by voltage division with Rsc and Rin,CE

$$|v_{in,CE}| = \frac{R_{in,CE}}{R_{in,CE} + R_{sc}} |v_{sc}| = 5.11mV$$

$$A_{v,CE} = \frac{v_{o,CE}}{v_{in,CE}} = -G_{m,CE} (R_{out,CE} \parallel R_{in,buf}) = -0.04(1923.08\Omega \parallel 2k\Omega) = -73.71V/V$$

$$A_{v,buf} = 0.8553V/V$$

$$|v_{out}| = A_{v,CE} A_{v,buf} |v_{in,CE}| = 322.35mV$$

$$b) R_{in,Q1E} = 2000 \parallel \frac{50k\Omega + (2000 \parallel R_{in,buf})}{2001} = 25.611\Omega$$

$$R_{in,Q1E} = 25.611\Omega \quad \text{Resistance seen looking into emitter of Q1 in Question 2}$$

If ro is much larger than Rc and RL, you may use the following equation:

$$R_{in,Q1E} = r_{\pi1} \parallel \frac{r_{o1}}{g_{m1} r_{o1} + 1} = 24.68\Omega$$

Notice that load resistance has a much larger effect on Rin compared to CE Amplifier.

Input of the CE amplifier is determined by voltage division with Rsc and Rin,CE

Don't ignore effects of Rc and RL in CB amplifier.

$$R_{in,CB} = R_{in,Q1E} \parallel R_E = 25.611\Omega \parallel 250\Omega = 23.23\Omega$$

$$|v_{in,CB}| = \frac{R_{in,CB}}{R_{in,CB} + R_{sc}} |v_{sc}| = 444\mu V$$

$$A_{v,CB} = \frac{v_{o,CB}}{v_{in,CB}} = -G_{m,CB} (R_{out,CB} \parallel R_{in,buf}) = -0.04002(1923.08\Omega \parallel 44.12k\Omega) = 73.75V/V$$

$$A_{v,buf} = 0.8553V/V$$

$$|v_{out}| = A_{v,CB} A_{v,buf} |v_{in,CB}| = 28.00mV$$

- c) Input signal applied to the CB amplifier is much weaker than input voltage of the CE amplifier. This is because of small input resistance of the CB amplifier. Voltage divider ratio is very small in CB case.

5)