$$I_{0} = \frac{k_{0}}{2} \cdot \frac{W}{L} \cdot (V_{GS} - V_{Thp})^{2} \cdot \left(1 + \frac{V_{OS}}{VA}\right)$$

$$0.2 \text{ mA} = \frac{k_{0}}{2} \cdot 10^{-6} \cdot \frac{20}{14} \cdot (V_{GS} + 0.8)^{2} \cdot \left(1 + \frac{V_{OS}}{40}\right)$$

$$0.5 = (V_{G} - 3 + 0.8)^{2} \cdot \left(1 + \frac{V_{0} - 3}{40}\right)$$

$$V_{D7} = V_{S1} = V_{S2}$$